

회로 이론 I

12년 중간고사


07명동주

① 저항값 오차


저항값	0	1	2	3	4	5	6	7	8	9
정	갈	빨	주	노	초	파	보	회	흰	
오차	$\pm 5\%$	$\pm 10\%$								
	2	0								

$$25 \times 10^3 [\Omega] \pm 5\%$$

② 등가저항 R_{ab} , R_{cd}

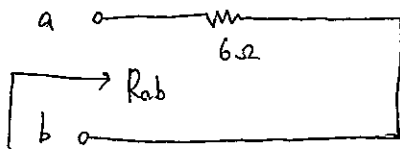


$$R_{ab} = 6 \Omega$$

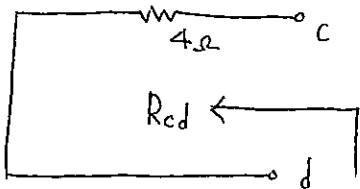

$$R_{cd} = 4 \Omega$$

* ③ ~ ④

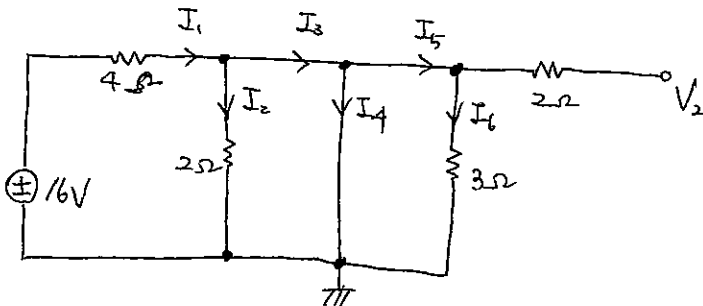

$$\textcircled{3} I_1 = \frac{16}{4} = 4A$$

$$I_4 = 4A$$

$$I_2 = 0A$$


$$I_5 = 0A$$

$$I_3 = 4A$$

$$I_6 = 0A$$

$$\textcircled{4} V_1 = 0V, V_2 = 0V$$

* ⑤ ~ ⑨

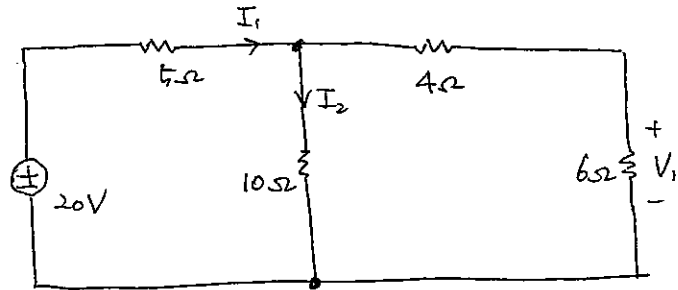

$$\begin{aligned} \textcircled{5} R_{eq} &= 5 + (10 \parallel (4+b)) \\ &= 5 + (10 \parallel 10) \\ &= 5 + 5 \\ &= 10 \end{aligned}$$

$$I_1 = \frac{20}{R_{eq}} = \frac{20}{10} = 2A$$


$$\textcircled{6} I_2 = I_1 \times \frac{(4+b)}{10 + (4+b)} = 2 \times \frac{1}{2} = 1A$$

$$\begin{aligned} \textcircled{7} V_1 &= (I_1 - I_2) \times 6 \Omega \\ &= (2 - 1) \times 6 = 6V \end{aligned}$$

$$\begin{aligned} \textcircled{8} P &= I^2 R \quad \text{전력} \\ &= 1^2 \times 10 = 10 [W] \end{aligned}$$

$$\begin{aligned} \textcircled{9} W &= P \cdot t \quad \text{에너지} \\ &= 10 \times 10 = 100 [J] \end{aligned}$$

* ⑩ ~ ⑫

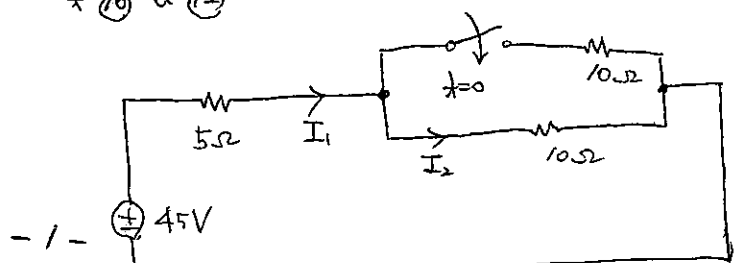


⑩ $t < 0$ 에서 $I_1 = \frac{45}{5+10} = 3[A]$
 $t > 0$ 에서 $I_1 = \frac{45}{5+(10//10)} = \frac{9}{2}[A]$

$I_1, t < 0 : I_2, t > 0 = 2:3$


⑪ $t < 0$ 에서 $I_2 = I_1 = 3A$
 $t > 0$ 에서 $I_2 = I_1 \times \frac{10}{10+10} = \frac{9}{2} \times \frac{1}{2} = \frac{9}{4}A$
 $I_2, t < 0 : I_2, t > 0 = 4:3$

⑫ $t < 0$ 에서 $P = I^2 R = 3^2 \times 5 = 45[W]$
 $t > 0$ 에서 $P = I^2 R = \left(\frac{9}{2}\right)^2 \times 5 = \frac{405}{4}[W]$
 $P, t < 0 : P, t > 0 = 4:9$

* ⑬ ~ ⑭

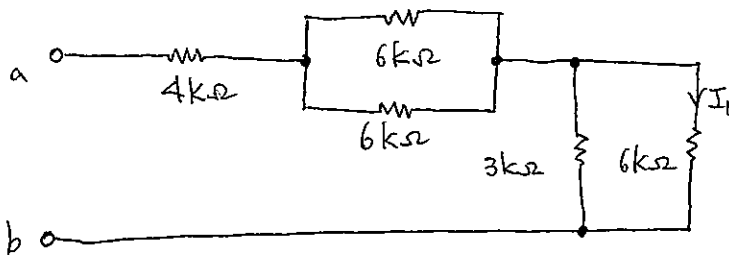

⑬ 전압원 연결. → 직렬

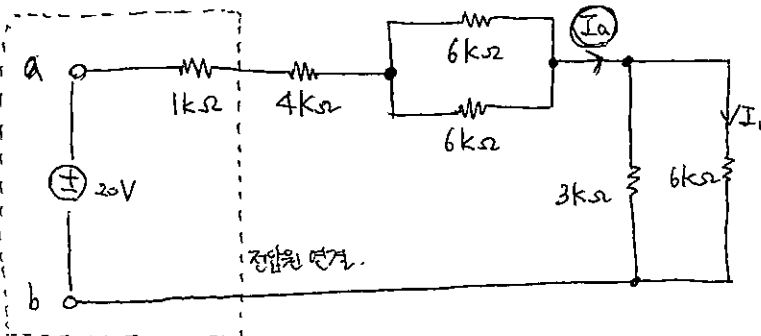


$Req = 1 + 4 + (6//6) + (3//6)$
 $= 10[k\Omega]$

$I_a = \frac{20}{10k} = 2[mA]$

$\therefore I_1 = I_a \times \frac{3k}{3k+6k} = 2mA \times \frac{1}{3} = \frac{2}{3}[mA]$


⑭ 전류원 연결 → 병렬

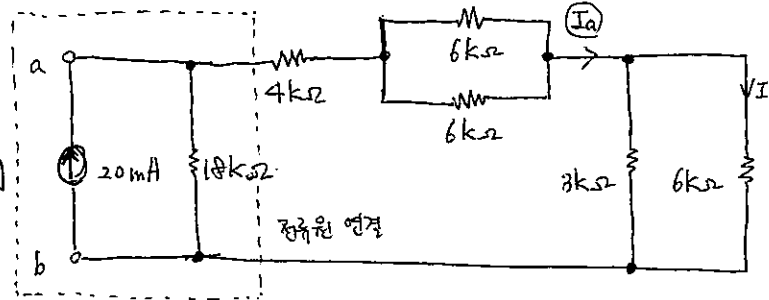


$I_a = 20mA \times \frac{10k}{10k + 9k} = \frac{40}{3}[mA]$

$\therefore I_1 = I_a \times \frac{3k}{3k+6k} = \frac{40}{3}mA \times \frac{1}{3} = \frac{40}{9}[mA]$
 $9k = 4k + (6k//6k) + (3k//6k)$


* ⑮ ~ ⑯

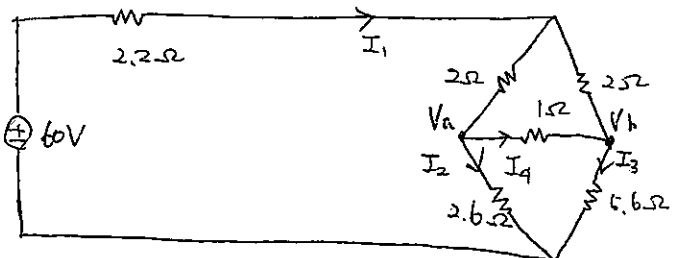

⑮ 등가저항 Req.

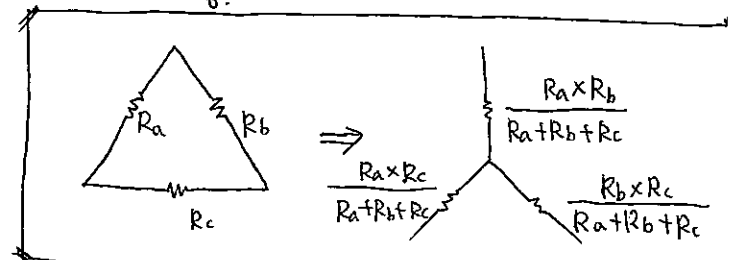

등가회로

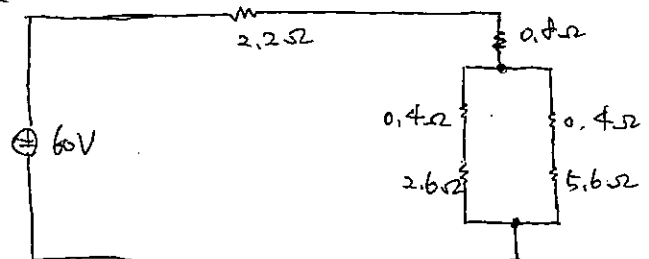

$$\begin{aligned}\therefore R_{eq} &= 2.2 + 0.8 + ((0.4+2.6) // (0.4+5.6)) \\ &= 3 + (3 // 6) \\ &= 5 [\Omega]\end{aligned}$$

$$\begin{aligned}V_o &= \frac{28}{5} \\ \therefore I_o &= V_o \times \frac{1}{6} = \frac{28}{5} \times \frac{1}{6} \\ &= \frac{13}{5} [A]\end{aligned}$$

$$\begin{aligned}(16) \quad I_1 &= \frac{60V}{R_{eq}} = \frac{60}{5} = 12[A] \\ I_2 &= 12 \times \frac{6}{3+6} = 12 \times \frac{2}{3} = 8[A] \\ I_3 &= 12 \times \frac{3}{3+6} = 12 \times \frac{1}{3} = 4[A]\end{aligned}$$

(17) (1Ω의 양단을 V_a, V_b 라 잡았을 때)


$$I_4 = \frac{V_a - V_b}{R}$$

여기서 $V_a = I_2 \times 2.6 = 8 \times 2.6 = \frac{104}{5} [V]$

$V_b = I_3 \times 5.6 = 4 \times 5.6 = \frac{112}{5} [V]$

$$\therefore I_4 = \frac{\frac{104}{5} - \frac{112}{5}}{1\Omega} = -\frac{8}{5} [A]$$

* (16) ~ (22)

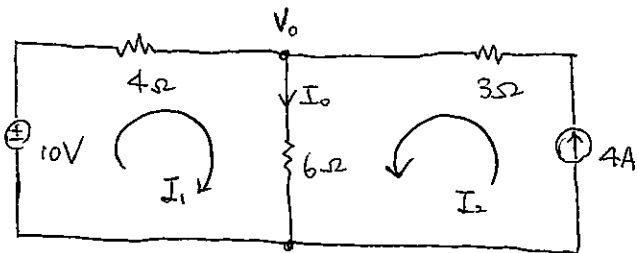

(18) 마디 해석법.

$$I_o = \frac{V_o}{6}$$

KCL 적용

$$\frac{10 - V_o}{4} + 4 = \frac{V_o}{6}$$

$$30 - 3V_o + 48 = 2V_o$$

$$6V_o = 78$$

(19) 루프 해석법

$$I_o = I_1 + I_2 = I_1 + 4$$

$$(\because I_2 = 4A)$$

KVL 적용.

$$10 = 4I_1 + 6(I_1 + 4)$$

$$10I_1 + 24 = 10$$


$$10I_1 = -14$$

$$I_1 = -\frac{2}{5} A$$

$$\therefore I_o = I_1 + 4 = -\frac{2}{5} + \frac{20}{5} = \frac{18}{5} [A]$$


(20) 중첩의 원리

i) 전압원만 있을 때. (전원 open)

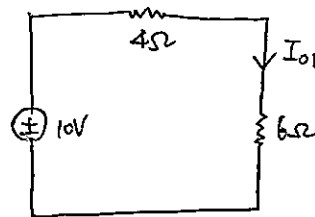

$$I_{o1} = \frac{10}{10} = 1A$$

ii) 전류원만 있을 때 (전압원 close)

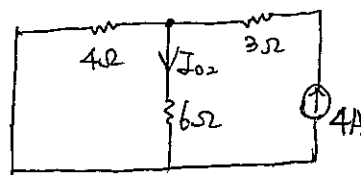


$$\begin{aligned}I_{o2} &= 4 \times \frac{4}{6+4} \\ &= \frac{8}{5} A\end{aligned}$$

$$\therefore I_o = I_{o1} + I_{o2} = 1 + \frac{8}{5} = \frac{13}{5} [A]$$


㉑ 테브난의 정리.

i) R_{TH}

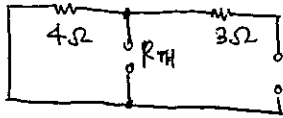


$$R_{TH} = 4\Omega$$

ii) V_{OC1}

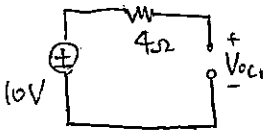

$$V_{OC1} = 10V$$


iii) V_{OC2}

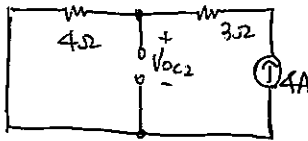

$$V_{OC2} = 4 \times 4 = 16V$$

$$\therefore V_{OC} = 10 + 16 = 26V$$


테브난의 등가회로.

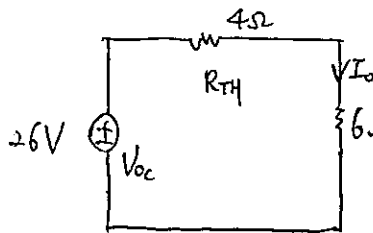

$$\therefore I_O = \frac{26}{10} = \frac{13}{5} [A]$$


㉒ 노턴의 정리

i) I_{SC1}

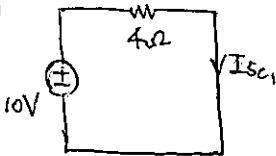

$$I_{SC1} = \frac{10}{4} = \frac{5}{2} A$$


ii) I_{SC2}

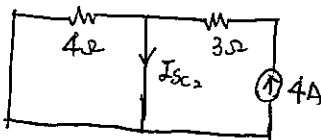

$$I_{SC2} = 4A$$


$$\therefore I_{SC} = \frac{5}{2} + 4 = \frac{13}{2} A$$

노턴의 등가회로

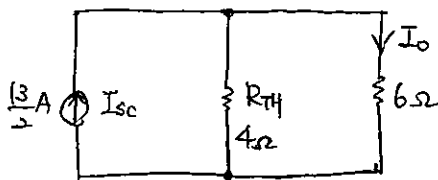

$$\therefore I_O = \frac{13}{2} \times \frac{4}{4+6} = \frac{13}{5} [A]$$

* ㉓ ~ ㉔

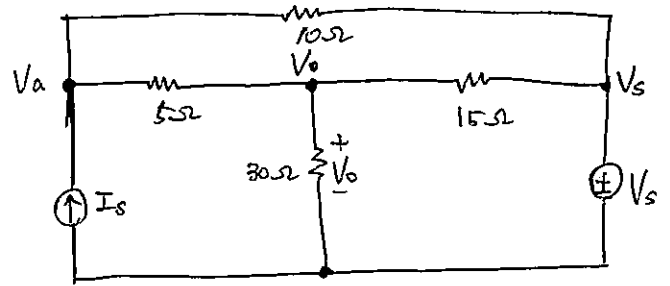

㉓ 마디해석법

V_O 에서 KCL 적용.

$$\frac{V_a - V_O}{5} + \frac{V_S - V_O}{15} = \frac{V_O}{30}$$

$$6V_a - 6V_O + 2V_S - 2V_O = V_O$$

$$9V_O = 6V_a + 2V_S \quad \dots \textcircled{1}$$

V_a 에서 KCL 적용

$$I_S = \frac{V_a - V_O}{5} + \frac{V_a - V_S}{10}$$

$$10I_S = 2V_a - 2V_O + V_a - V_S$$


$$2V_O = 3V_a - V_S - 10I_S \quad \dots \textcircled{2}$$

㉑ - ㉒ $\times 2$ 를 하면

$$\begin{aligned} 9V_O &= 6V_a + 2V_S \\ -4V_O &= 6V_a - 2V_S - 20I_S \end{aligned}$$

$$5V_O = 4V_S + 20I_S$$
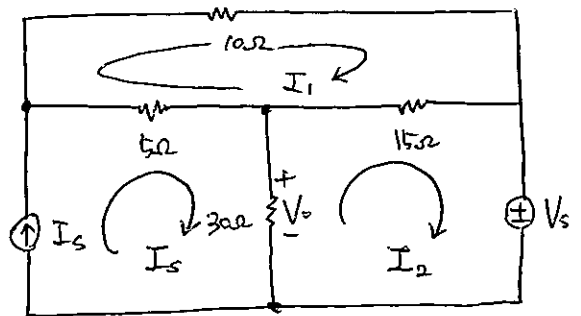
$$\therefore V_O = \frac{4}{5}V_S + 4I_S$$



㉔ 루프해석법

$$V_O = 30(I_S - I_2)$$

I_1 에서 KVL 적용

$$5(I_1 - I_S) + 10I_1 + 15(I_1 - I_2) = 0$$

$$30I_1 - 15I_2 = 5I_S \quad \dots \textcircled{1}$$

I_2 에 KVL 적용

$$30(I_2 - I_5) + 15(I_2 - I_1) + V_5 = 0$$

$$-15I_1 + 45I_2 = -V_5 + 30I_5 \quad \dots \textcircled{2}$$

① + ② × 2 를 하면

$$\begin{array}{r} 30I_1 - 15I_2 = 5I_5 \\ + \quad -30I_1 + 90I_2 = -2V_5 + 60I_5 \\ \hline 75I_2 = -2V_5 + 65I_5 \end{array}$$


$$I_2 = -\frac{2}{75}V_5 + \frac{13}{15}I_5$$

$$\therefore V_0 = 30(I_5 + \frac{2}{75}V_5 - \frac{13}{15}I_5)$$

$$= \frac{4}{5}V_5 + 4I_5$$


㉔ 중첩의 원리

i) 전압원만 있을 때

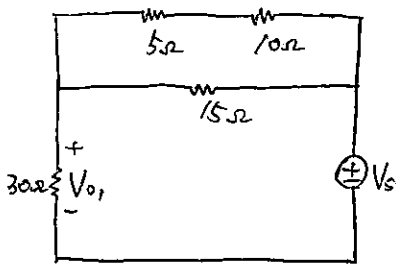

$$\begin{aligned} V_{01} &= V_s \times \frac{30}{30 + \frac{15}{2}} \\ &= \frac{4}{5}V_s \end{aligned}$$

ii) 전류원만 있을 때

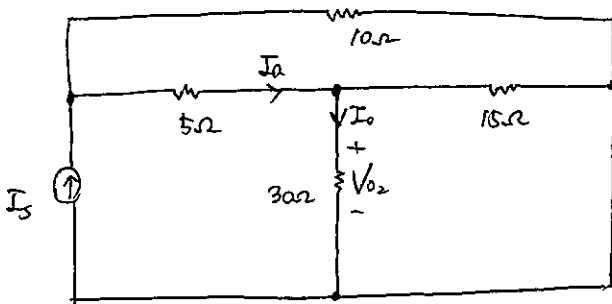

$$V_{02} = 30I_0$$

$$I_a = I_s \times \frac{10}{10 + (5 + (30 \parallel 15))} = \frac{2}{5}I_s$$


$$I_0 = \frac{2}{5}I_s \times \frac{15}{30 + 15} = \frac{2}{75}I_s$$

$$V_{02} = 30 \times \frac{2}{75}I_s = 4I_s$$

$$\therefore V_0 = V_{01} + V_{02} = \frac{4}{5}V_s + 4I_s$$


㉔ 테브난의 정리

i) R_{TH}

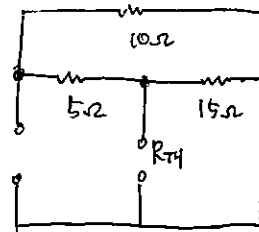


$$\begin{aligned} R_{TH} &= (5 + 10) \parallel 15 \\ &= \frac{15}{2} \Omega \end{aligned}$$

ii) V_{OC1}

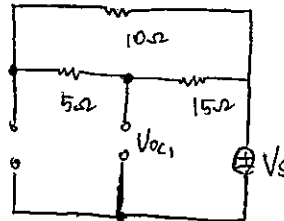

$$V_{OC1} = V_s$$

iii) V_{OC2}

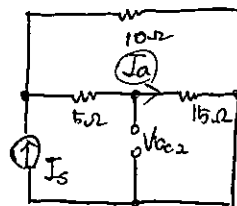


$$V_{OC2} = I_a \times 15$$

$$\begin{aligned} I_a &= I_s \times \frac{10}{10 + (5 + 15)} \\ &= \frac{1}{3}I_s \end{aligned}$$

$$V_{OC2} = 5I_s$$

$$\therefore V_{OC} = V_{OC1} + V_{OC2} = V_s + 5I_s$$


• 테브난의 등가회로

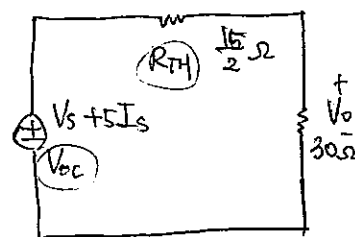

$$\therefore V_0 = (V_s + 5I_s) \times \frac{30}{\frac{15}{2} + 30} = \frac{4}{5}V_s + 4I_s$$


27) 노턴의 정리

i) I_{sc1}

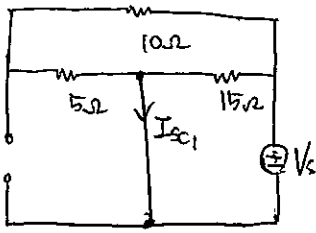

$$I_{sc1} = \frac{V_s}{\frac{15}{2}} = \frac{2}{15} V_s$$

ii) I_{sc2}

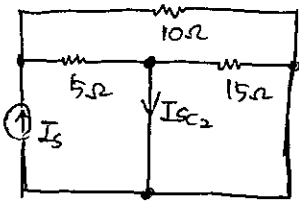


$$I_{sc2} = I_s \times \frac{10}{5+10} = \frac{2}{3} I_s$$

* 15Ω의 저항은 전류 32A ×

$$\therefore I_{sc} = \frac{2}{15} V_s + \frac{2}{3} I_s$$

• 노턴의 등가회로

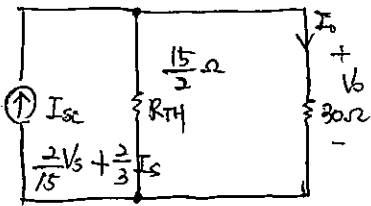


$$V_o = 30 I_o$$

$$I_o = I_{sc} \times \frac{\frac{15}{2}}{\frac{15}{2} + 30}$$

$$\therefore V_o = 30 \times \left(\frac{2}{15} V_s + \frac{2}{3} I_s \right) \times \frac{\frac{15}{2}}{\frac{15}{2} + 30}$$

$$= \frac{4}{5} V_s + 4 I_s$$

* 28) ~ 32)

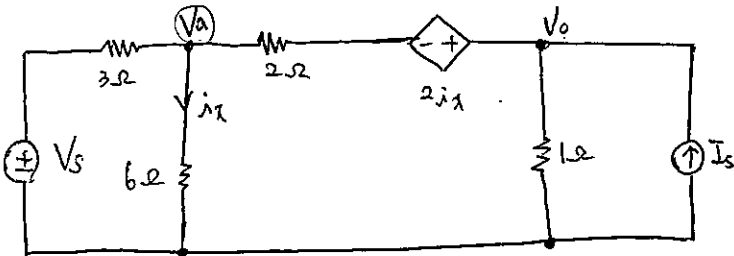

28) 마디해석법

$$i_1 = \frac{V_a}{6}$$

V_a 에서 KCL 적용

$$\frac{V_s - V_a}{3} = \frac{V_a}{6} + \frac{V_a - (V_o - 2i_1)}{2}$$

$$2V_s - 2V_a = V_a + 3V_a - 3V_o + V_a$$

$$7V_a - 3V_o = 2V_s \quad \dots \textcircled{1}$$

V_o 에서 KCL 적용

$$\frac{V_a - (V_o - 2i_1)}{2} + I_s = \frac{V_o}{1}$$

$$V_a - V_o + \frac{1}{3} V_a + 2I_s = 2V_o$$

$$\frac{4}{3} V_a - 3V_o = -2I_s$$

$$4V_a - 9V_o = -6I_s \quad \dots \textcircled{2}$$

$$(\textcircled{1} \times 4) - (\textcircled{2} \times 1)$$


$$28V_a - 12V_o = 8V_s$$

$$28V_a - 63V_o = -42I_s$$

$$5V_o = 8V_s + 42I_s$$

$$\therefore V_o = \frac{8}{5} V_s + \frac{14}{1} I_s$$

29) 전류해석법

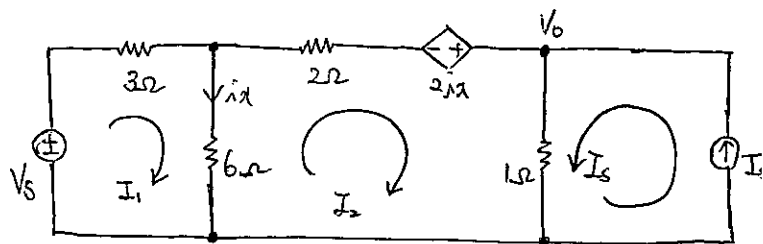

$$i_1 = I_1 - I_2, \quad V_o = 1 \times (I_2 + I_s)$$

I_1 에서 KVL 적용

$$V_s = 3I_1 + 6(I_1 - I_2)$$

$$9I_1 - 6I_2 = V_s \quad \dots \textcircled{1}$$

$$6(I_2 - I_1) + 2I_2 - 2i_1 + I_2 + I_s = 0$$

$$6I_2 - 6I_1 + 2I_2 - 2I_1 + 2I_2 + I_2 + I_s = 0$$

$$-8I_1 + 11I_2 = -I_s \quad \dots \textcircled{2}$$


(①×8) + (②×9) 을 할 때

$$\begin{aligned}
 & 12I_1 - 48I_2 = 8V_s \\
 + & \left| \begin{aligned} -12I_1 + 99I_2 &= -9I_s \end{aligned} \right. \\
 \hline
 & 51I_2 = 8V_s - 9I_s \\
 & I_2 = \frac{8}{51}V_s - \frac{9}{51}I_s
 \end{aligned}$$

$$\begin{aligned}
 \therefore V_o &= \frac{8}{51}V_s - \frac{9}{51}I_s + I_s \\
 &= \frac{8}{51}V_s + \frac{14}{17}I_s
 \end{aligned}$$

③ 중첩의 원리.

i) 전압원만 있을 때

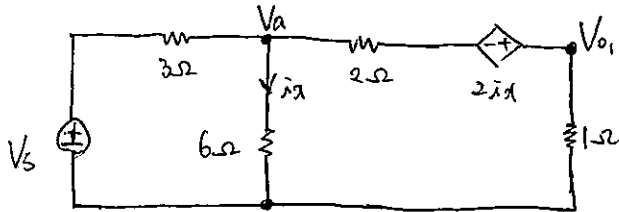

Va에서 KCL 적용

$$\frac{V_s - V_a}{3} = \frac{V_a}{6} + \frac{V_a - (V_{o1} - 2j1x)}{2}$$

$$\begin{aligned}
 2V_s - 2V_a &= V_a + 3V_a - 3V_{o1} + V_a \\
 &(\because j1x = \frac{1}{6}V_a)
 \end{aligned}$$

$$1V_a - 3V_{o1} = 2V_s \quad \dots ①$$

$$\frac{V_a - (V_{o1} - 2j1x)}{2} = \frac{V_{o1}}{1}$$

$$V_a - V_{o1} + \frac{1}{3}V_a = 2V_{o1}$$


$$\frac{4}{3}V_a - 3V_{o1} = 0$$

$$4V_a - 9V_{o1} = 0 \quad \dots ②$$

(①×4) - (②×9) 을 할 때

$$\begin{aligned}
 & 28V_a - 12V_{o1} = 8V_s \\
 - & \left| \begin{aligned} 28V_a - 63V_{o1} &= 0 \end{aligned} \right. \\
 \hline
 & 51V_{o1} = 8V_s \\
 \therefore V_{o1} &= \frac{8}{51}V_s
 \end{aligned}$$

ii) 전류원만 있을 때

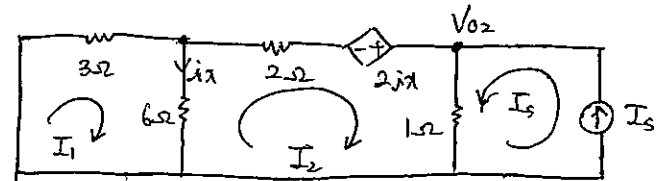

$$i_x = I_1 - I_2, \quad V_{o2} = 1 \times (I_2 + I_s)$$

I1에서 KVL 적용

$$3I_1 + 6(I_1 - I_2) = 0.$$

$$9I_1 - 6I_2 = 0 \quad \dots ①$$

I2에서 KVL 적용

$$6(I_2 - I_1) + 2I_2 - 2j1x + I_2 + I_s = 0.$$

$$6I_2 - 6I_1 + 2I_2 - 2I_1 + 2I_2 + I_2 + I_s = 0$$

$$-8I_1 + 11I_2 = -I_s \quad \dots ②$$

(①×8) + (②×9) 을 할 때


$$\begin{aligned}
 & 12I_1 - 48I_2 = 0 \\
 + & \left| \begin{aligned} -12I_1 + 99I_2 &= -9I_s \end{aligned} \right. \\
 \hline
 & 51I_2 = -9I_s \\
 I_2 &= -\frac{9}{51}I_s
 \end{aligned}$$

$$V_{o2} = -\frac{9}{51}I_s + I_s = \frac{14}{17}I_s$$

$$\therefore V_o = V_{o1} + V_{o2} = \frac{8}{51}V_s + \frac{14}{17}I_s$$

③) u ④) V_{oc} , I_{sc} , R_{TH} 찾기.

- V_{oc} 찾기.

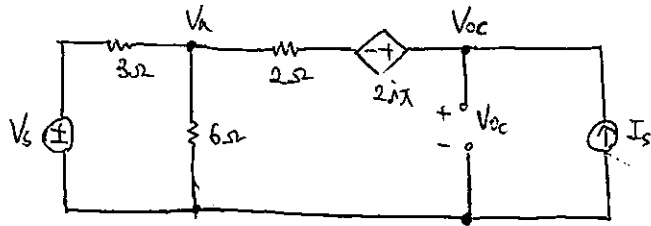

V_a 에 KCL 적용

$$\frac{V_s - V_a}{3} = \frac{V_a}{6} + \frac{V_a - (V_{oc} - 2i_x)}{2}$$

$$2V_s - 2V_a = V_a + 3V_a - 3V_{oc} + 4V_a$$

$$(\because i_x = \frac{1}{6}V_a)$$

$$1V_a - 3V_{oc} = 2V_s \quad \dots ①$$

V_{oc} 에 KCL 적용

$$\frac{V_a - (V_{oc} - 2i_x)}{2} + I_s = 0.$$

$$V_a - V_{oc} + \frac{1}{3}V_a = -2I_s$$

$$\frac{4}{3}V_a - V_{oc} = -2I_s$$

$$4V_a - 3V_{oc} = -6I_s \quad \dots ②$$


(① × 4) - (② × 1) 을 할 때

$$\begin{array}{r} 24V_a - 12V_{oc} = 4V_s \\ -4V_a + 3V_{oc} = 6I_s \\ \hline 20V_a - 9V_{oc} = 4V_s + 6I_s \end{array}$$

$$9V_{oc} = 42I_s + 4V_s$$

$$\therefore V_{oc} = \frac{4}{9}V_s + \frac{14}{3}I_s.$$

- I_{sc} 찾기

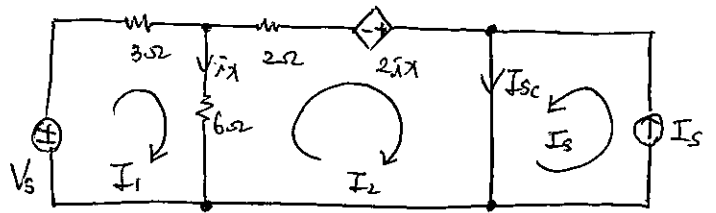

$$i_x = I_1 - I_2, \quad I_{sc} = I_2 + I_s$$

I_1 에 KVL 적용

$$V_s = 3I_1 + 6(I_1 - I_2)$$

$$9I_1 - 6I_2 = V_s \quad \dots ①$$

I_2 에 KVL 적용

$$6(I_2 - I_1) + 2I_2 - 2i_x = 0$$

$$6I_2 - 6I_1 + 2I_2 - 2I_1 + 2I_2 = 0$$

$$-4I_1 + 10I_2 = 0 \quad \dots ②$$

(① × 4) + (② × 9) 을 할 때

$$36I_1 - 24I_2 = 4V_s$$

$$+ \quad \begin{array}{r} -36I_1 + 90I_2 = 0 \\ \hline 66I_2 = 4V_s \end{array}$$

$$I_2 = \frac{4}{21}V_s$$

$$\therefore I_{sc} = \frac{4}{21}V_s + I_s.$$


- R_{TH} 찾기

$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{4}{9}V_s + \frac{14}{3}I_s}{\frac{4}{21}V_s + I_s}$$

$$= \frac{\frac{14}{3} \left(\frac{4}{9}V_s + \frac{14}{3}I_s \right)}{\left(\frac{4}{21}V_s + I_s \right)} = \frac{14}{3} \Omega$$

㉓) 테브난의 정리

• 테브난의 등가회로.

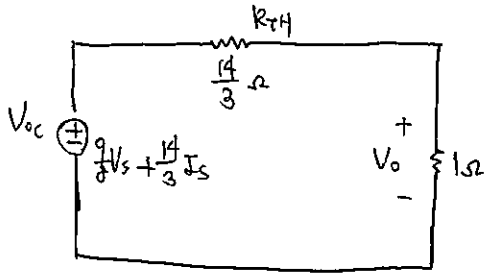


$$V_o = \left(\frac{9}{8} V_s + \frac{14}{3} I_s \right) \times \frac{1}{\frac{14}{3} + 1}$$

$$= \frac{8}{51} V_s + \frac{14}{17} I_s$$

㉔) 노턴의 정리

• 노턴의 등가회로.

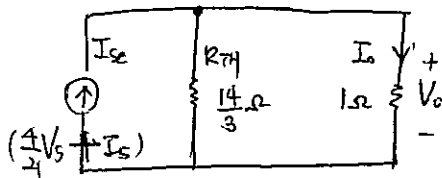


$$V_o = 1 \times I_o = I_o$$

$$I_o = I_{sc} \times \frac{\frac{14}{3}}{\frac{14}{3} + 1}$$

$$\therefore V_o = \left(\frac{4}{21} V_s + I_s \right) \times \frac{\frac{14}{3}}{\frac{14}{3} + 1}$$


$$= \frac{8}{51} V_s + \frac{14}{17} I_s$$

✗ ㉓) ~ ㉔)

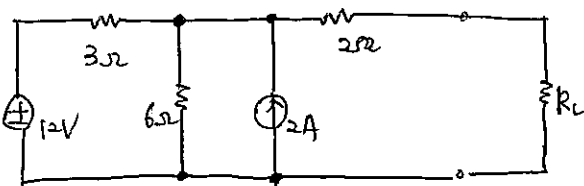

㉕) 최대전력 위한 R_L 값

$R_{TH} = R_L$ 일때 최대전력이 전달 됨.

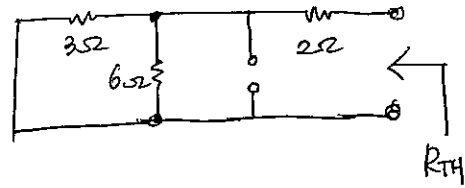


$$R_{TH} = 2 + (3//6) = 2 + 2 = 4 \Omega$$

$\therefore R_L = 4 \Omega$ 일때 최대전력.

㉖) R_L에 최대전력.


$$P_{L/\max} = \frac{V_{oc}^2}{4 R_{TH}}$$

i) V_{oc1}

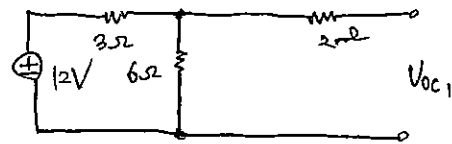

$$V_{oc1} = 12 \times \frac{6}{3+6} = 8 V$$

ii) V_{oc2}

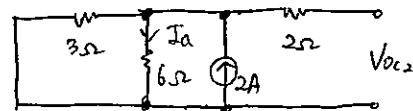


$$V_{oc2} = 6 \times I_a$$

$$= 6 \times 2 \times \frac{3}{3+6} = 4 V$$

$$\therefore V_{oc} = 8 + 4 = 12 V$$

$$\therefore P_{L/\max} = \frac{12^2}{4 \times 4} = 9 [W]$$


* 35 ~ 38

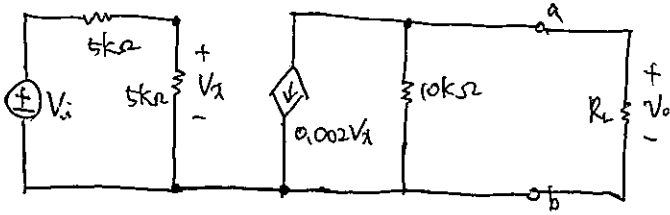

$$\therefore \text{전압이득 } A_v = \frac{V_o}{V_i} = \frac{-5V_i}{V_i} = \boxed{-5}$$

수고하셨습니다. 좋은 결과 있으시길 ... ^^

36) i) R_{TH}

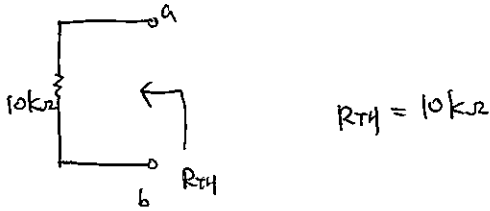

$$R_{TH} = 10k\Omega$$


ii) V_{oc}

$$V_{oc} = -0.002 V_1 \times 10k = -20V_1$$

$$= -20 \times \frac{5k}{5k+5k} V_i$$

$$= -10V_i$$

오버브로잉의 등가회로

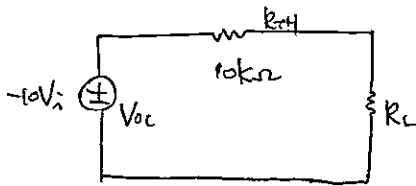

36) 최대전력 전달을 위해선 $R_L = R_{TH}$ 이어야 하므로.

$$R_L = 10[k\Omega]$$

37) 최대전력

$$P_{L/\max} = \frac{V_{oc}^2}{4 \cdot R_{TH}} = \frac{(-10V_i)^2}{4 \times 10k} = 2.5V_i^2 [mW]$$

38) 전압이득

$$V_o = -10V_i \times \frac{10k}{10k+10k} = -5V_i$$

회로 이론 I

12년 기말고사

이명동주

① 저항값. E차.

저항값	0	1	2	3	4	5	6	7	8	9
	검	갈	빨	주	노	초	파	보	회	흑
E차	$\pm 5\%$	$\pm 10\%$								
	중	은								

$$25 \times 10^4 [\Omega] \pm 5\%$$



② capacitor 용량. E차.



$$22 \times 10^2 [\text{pF}] \pm 5\%$$


1H	: 50V (정격전압을 4타입)
222	: $\boxed{22} \times 10^{\boxed{2}} [\text{pF}]$
	↑ 앞 두자리 ↑ 뒷 한자리
J	: 오차 $\pm 5\%$ $\pm 10\%$ $\pm 20\%$
	J K M

③ 등가저항 R_{ab} , R_{cd}

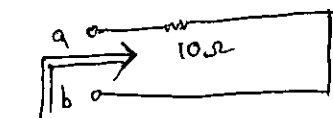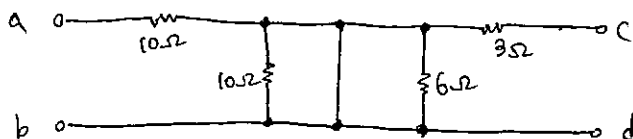


$$R_{ab} = 10\Omega$$

$$R_{cd} = 3\Omega$$

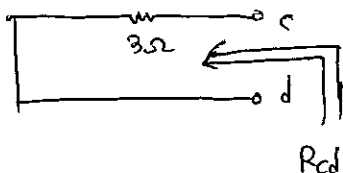


④ 등가 인덕턴스 L_{eq} 는?

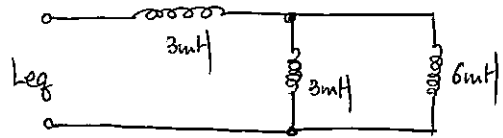

$$L_{eq} = 3 \text{ mH} + (3 \text{ mH} \parallel 6 \text{ mH})$$

$$= 3 \text{ mH} + 2 \text{ mH} = 5 [\text{mH}]$$


⑤ 등가 capacitance. C_{eq} 는?

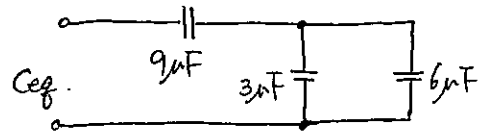

$$C_{eq} = 9 \mu\text{F} \parallel (3 \mu\text{F} + 6 \mu\text{F})$$

$$= 9 \mu\text{F} \parallel 9 \mu\text{F} = \frac{9}{2} [\mu\text{F}]$$

* ⑥ ~ ⑦

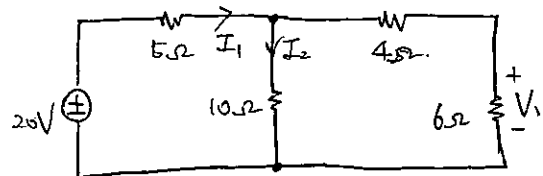

⑥ I_1 과 I_2 및 V_1 을 구하시오.

$$R_{eq} = 5 + (10 \parallel (6 + 4)) = 10\Omega$$

$$I_1 = \frac{V}{R_{eq}} = \frac{20}{10} = 2 [\text{A}]$$

$$I_2 = 2 \text{ A} \times \frac{10}{10 + 10} = 1 [\text{A}]$$

$$V_1 = 6 \times 1 = 6 [\text{V}]$$


⑦ $P = I^2 R$ 전력

$$W = P \cdot t \text{ 에너지}$$


$$P = 1^2 \times 10 = 10 [\text{W}]$$

$$W = 10 \times 10 = 100 [\text{J}]$$

* ⑧

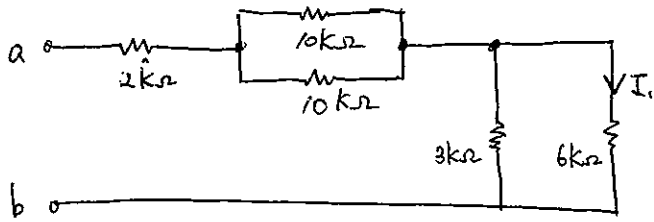

⑧ 전압원 연결.

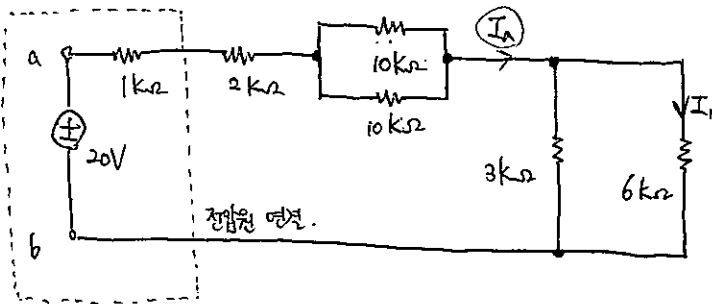


$$R_{eq} = 1k + 2k + (10k // 10k) + (3k // 6k) \\ = 10k\Omega.$$


$$I_A = \frac{20}{10k} = 2mA$$

$$I_1 = 2mA \times \frac{3k}{3k + 6k} = \frac{2}{3} [mA]$$


* ⑨ ~ ⑪

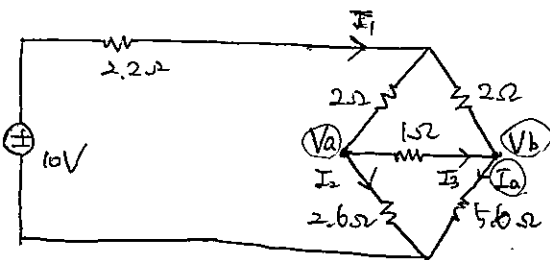

⑨ 등가저항 R_{eq}

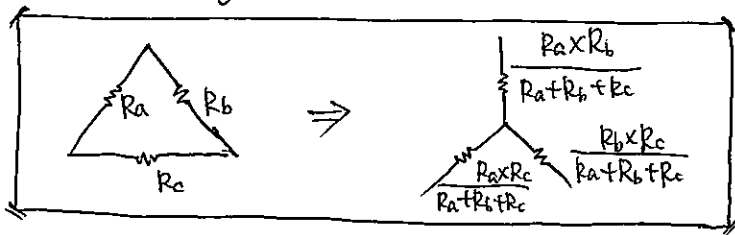

등가회로

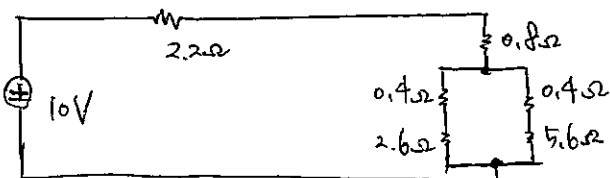

$$R_{eq} = 2.2 + 0.8 + ((0.4 + 2.6) // (0.4 + 5.6)) \\ = 3 + (3 // 6) \\ = 5 [\Omega]$$

⑩ I_1, I_2

$$I_1 = \frac{V}{R_{eq}} = \frac{10}{5} = 2 [A]$$

$$I_2 = 2A \times \frac{6}{3+6} = \frac{4}{3} [A]$$

⑪ I_3

$$I_a = 2A \times \frac{3}{3+6} = \frac{2}{3} A.$$


$$I_3 = \frac{V_a - V_b}{R}$$

$$\text{여기서 } V_a = I_2 \times 2.6 = \frac{4}{3} \times \frac{13}{5} = \frac{52}{15} V$$

$$V_b = I_a \times 5.6 = \frac{2}{3} \times \frac{28}{5} = \frac{56}{15} V$$

$$I_3 = \frac{\frac{52}{15} - \frac{56}{15}}{1\Omega} = -\frac{4}{15} [A]$$

* ⑫ ~ ⑬

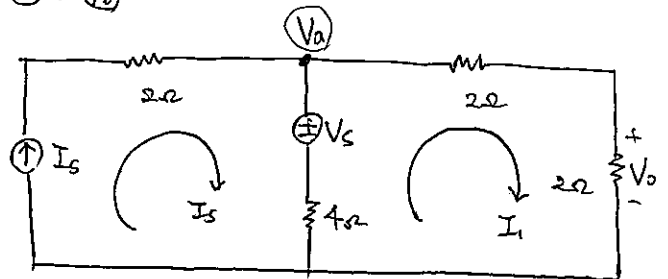

⑫ 마티세스법

$$V_o = \frac{2}{2+2} V_A = \frac{1}{2} V_A$$

V_A 에서 KCL 적용

$$I_s = \frac{V_A - V_s}{4} + \frac{V_A}{4}$$

$$4I_s = V_A - V_s + V_A$$

$$V_A = 2I_s + \frac{1}{2} V_s$$

$$\therefore V_o = \frac{1}{2} V_a = \frac{1}{2} (2I_s + \frac{1}{2} V_s)$$

$$= I_s + \frac{1}{4} V_s$$

⑬ 주파수 해석법

I_1 에서 KVL 적용

$$V_s = 4(I_1 - I_s) + 2I_1 + 2I_1$$

$$V_s = 8I_1 - 4I_s$$

$$I_1 = \frac{1}{8} I_s + \frac{1}{8} V_s \quad \dots \textcircled{1}$$


구하려는 V_o 는

$$V_o = 2I_1 \quad \dots \textcircled{2} \quad \text{이므로 대입하면}$$


$$\therefore V_o = 2(\frac{1}{8} I_s + \frac{1}{8} V_s) = I_s + \frac{1}{4} V_s$$

⑭ 중첩의 정리

i) 전압원만 있을 때 (전류원 open)

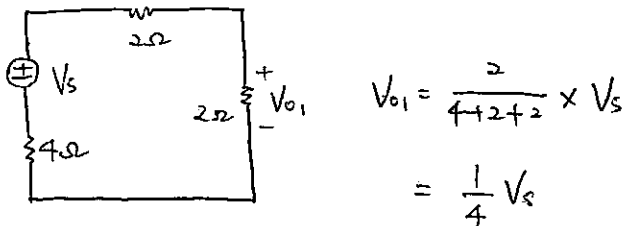

ii) 전류원만 있을 때 (전압원 close)

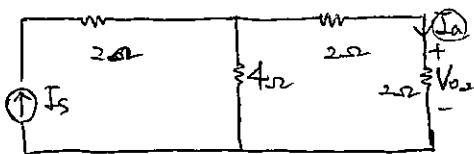


$$I_a = I_s \times \frac{4}{4+(2+2)} = \frac{1}{2} I_s$$

$$V_{o2} = 2 \cdot I_a = 2 \times \frac{1}{2} I_s = I_s$$


$$\therefore V_o = V_{o1} + V_{o2} = I_s + \frac{1}{4} V_s$$

⑮ 테브나지 정리


i) R_{TH}

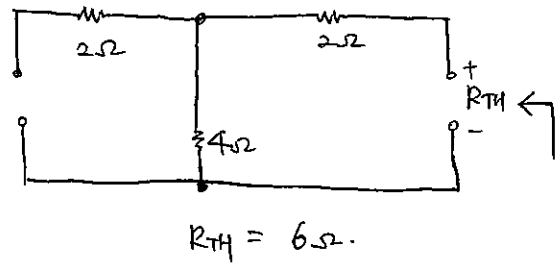


ii) V_{oc1}

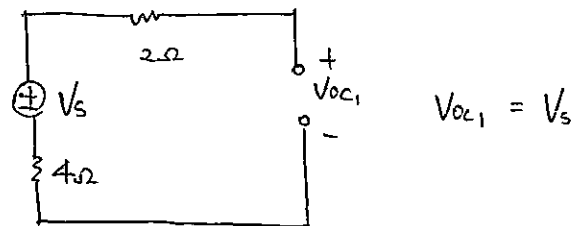

iii) V_{oc2}

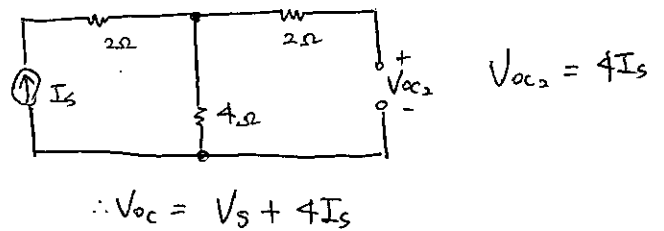

• 테브나지의 등가회로

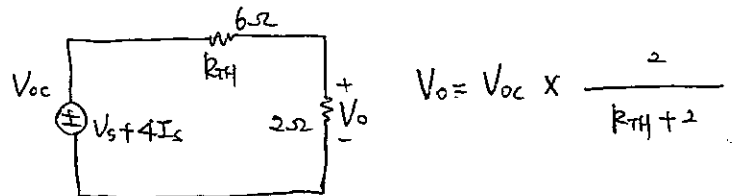


$$\therefore V_o = (V_s + 4I_s) \times \frac{2}{6+2}$$


$$= I_s + \frac{1}{4} V_s$$

⑯ 노턴의 정리

i) I_{sc1}

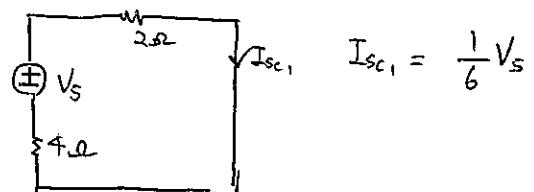


ii) I_{sc2}

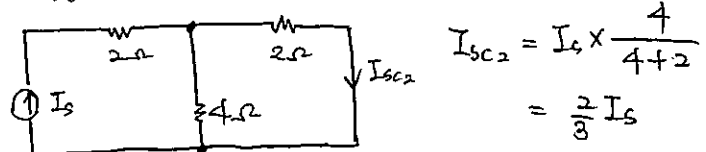

$$\therefore I_{sc} = \frac{1}{6} V_s + \frac{2}{3} I_s$$

이로부터 등가회로

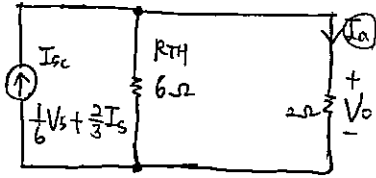

$$V_o = 2 \times I_a$$


$$I_a = I_{sc} \times \frac{6}{6+2}$$

$$= \frac{3}{4} I_{sc}$$

$$\therefore V_o = 2 \times \frac{3}{4} \times \left(\frac{1}{6} V_s + \frac{2}{3} I_s \right)$$


$$= I_s + \frac{1}{4} V_s$$

* 17 ~ 20

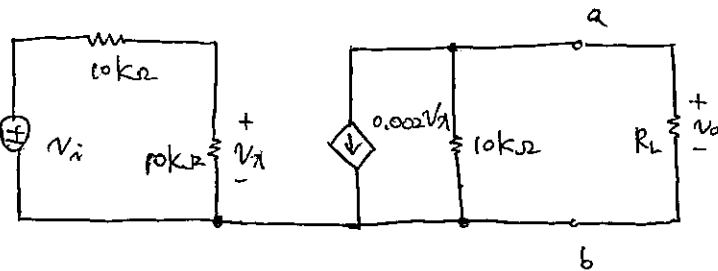

17 등가회로

i) R_{TH}

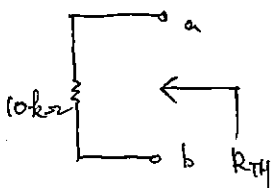

$$R_{TH} = 10k\Omega$$


ii) V_{oc}

$$V_{oc} = -0.002 V_i \times 10k = -20 V_i$$

$$= -20 \times \frac{10k}{10k+10k} V_i$$

$$= -10 V_i$$

이로부터 등가회로

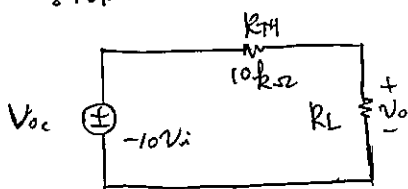

18 최대 전력 전달을 위해서는 $R_L = R_{TH}$ 이어야 함

$$R_L = 10[k\Omega]$$

19 최대 전력


$$P_{L/\max} = \frac{V_{oc}^2}{4 R_{TH}} = \frac{(-10 V_i)^2}{4 \times 10k} = 2.5 V_i^2 [mW]$$

20 전압이득


$$V_o = -10 V_i \times \frac{10k}{10k+10k} = -5 V_i$$

$$\therefore \text{전압이득 } A_v = \frac{V_o}{V_i} = \frac{-5 V_i}{V_i} = -5$$

* 21 ~ 22

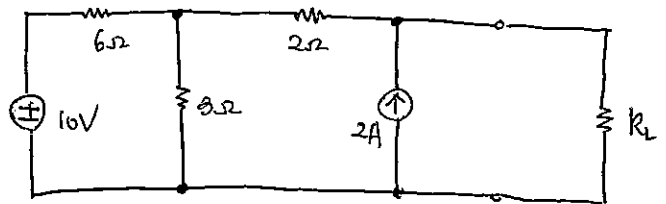

21 최대 전력 전달을 위한 R_L

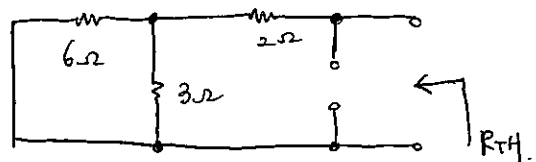


$$R_{TH} = 2 + (6/3) = 2 + 2 = 4[\Omega]$$

$$R_L = 4[\Omega] \text{ 일때 최대 전력}$$


22 최대 전력

i) V_{oc1}

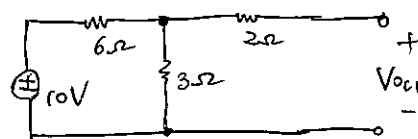

$$V_{oc1} = 10 \times \frac{3}{6+3} = \frac{10}{3} V$$

ii) V_{oc2}

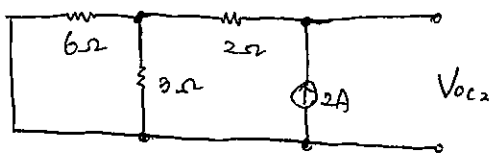


$$V_{oc2} = 2A \times (2 + (3//6))$$

$$= 8V$$

$$\therefore V_{oc} = V_{oc1} + V_{oc2} = \frac{10}{3}V + 8V = \frac{34}{3} [V]$$


• 테브낭의 등가회로

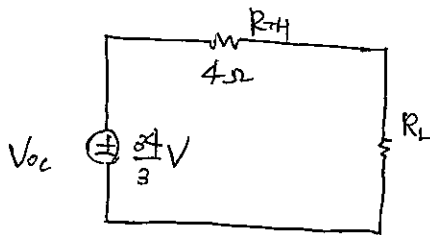


$$\therefore P_{Lmax} = \frac{V_{oc}^2}{4 \cdot R_{TH}} = \frac{(\frac{34}{3})^2}{4 \times 4} = 4.03$$

$$\doteq 4 [W]$$

* 23

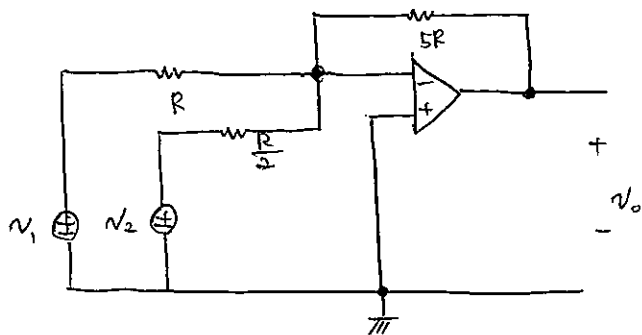


i) V_1 에 대하여

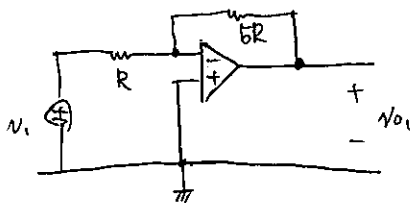

$$V_{o1} = -\frac{5R}{R} V_1$$

$$= -5V_1$$

ii) V_2 에 대하여

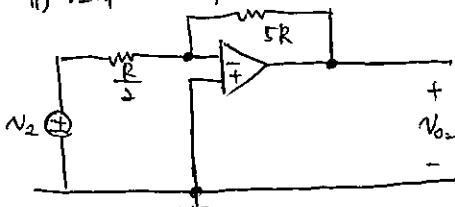


$$V_{o2} = -\frac{5R}{\frac{R}{2}} V_2$$

$$= -10V_2$$

$$\therefore V_o = V_{o1} + V_{o2} = -5V_1 - 10V_2$$

* 24

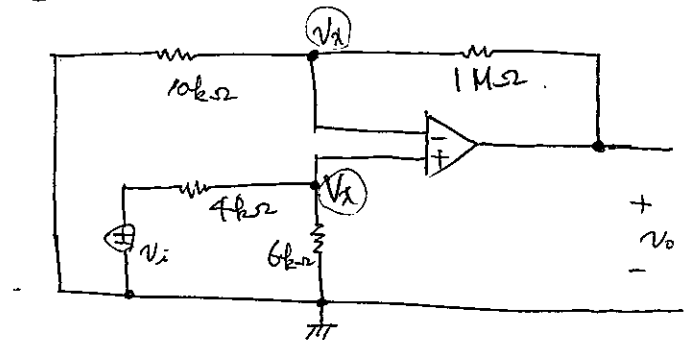

⊕장차에서

$$V_x = \frac{6k}{4k + 6k} V_i = \frac{3}{5} V_i \quad \dots ①$$

⊖단차에서

$$\frac{V_o - V_x}{1M} = \frac{V_x}{10k}$$

$$V_o = \frac{1M}{10k} V_x + V_x = 101 V_x \quad \dots ②$$

①을 ②에 대입.

$$V_o = 101 \times \frac{3}{5} V_i$$

$$\therefore \frac{V_o}{V_i} = \frac{303}{5}$$

* 25 ~ 27 Laplace 변환

$$25) \ddot{v}(t) + 3\dot{v}(t) + 2v(t) = 4u_s(t), \quad v(0) = \dot{v}(0) = 0$$

$$\xrightarrow{\mathcal{L}} s^2 V(s) + 3s V(s) + 2V(s) = \frac{4}{s}$$

$$V(s) = \frac{4}{s(s^2 + 3s + 2)} = \frac{4}{s(s+1)(s+2)}$$

$$= \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+2}$$

$$A = V(s) \times s \Big|_{s=0} = 2$$

$$B = V(s) \times (s+1) \Big|_{s=-1} = -4$$

$$C = V(s) \times (s+2) \Big|_{s=-2} = 2$$

$$\therefore V(s) = \frac{2}{s} + \frac{-4}{s+1} + \frac{2}{s+2}$$

$$\xrightarrow{\mathcal{L}^{-1}} v(t) = 2 - 4e^{-t} + 2e^{-2t}, \quad t \geq 0$$

$$\textcircled{26} \ddot{v}(t) + 4\dot{v}(t) + 4v(t) = 8u_s(t), v(0) = \dot{v}(0) = 0$$

$$\xrightarrow{\mathcal{L}} s^2 V(s) + 4sV(s) + 4V(s) = \frac{8}{s}$$

$$V(s) = \frac{8}{s(s^2 + 4s + 4)} = \frac{8}{s(s+2)^2}$$

$$= \frac{A}{s} + \frac{B}{(s+2)^2} + \frac{C}{s+2}$$

$$A = \frac{8}{s(s+2)^2} \times s \Big|_{s=0} = 2$$

$$B = \frac{8}{s(s+2)^2} \times (s+2)^2 \Big|_{s=-2} = -4$$

$$C = \frac{d}{ds} \left[\frac{8}{s(s+2)^2} \times (s+2)^2 \right] \Big|_{s=-2}$$

$$= \frac{d}{ds} \left[\frac{8}{s} \right] \Big|_{s=-2}$$

$$= \frac{-8}{s^2} \Big|_{s=-2} = -2$$

$$\therefore V(s) = \frac{2}{s} + \frac{-4}{(s+2)^2} + \frac{-2}{s+2}$$

$$\xrightarrow{\mathcal{L}^{-1}} v(t) = 2 - 4t \cdot e^{-2t} - 2e^{-2t}, t \geq 0$$

$$\textcircled{27} \ddot{v}(t) + 4\dot{v}(t) + 13v(t) = 26u_s(t), v(0) = \dot{v}(0) = 0$$

$$\xrightarrow{\mathcal{L}} s^2 V(s) + 4sV(s) + 13V(s) = \frac{26}{s}$$

$$V(s) = \frac{26}{s(s^2 + 4s + 13)}$$

$$= \frac{A}{s} + \frac{Bs + C}{s^2 + 4s + 13}$$

$$A = \frac{26}{s(s^2 + 4s + 13)} \times s \Big|_{s=0} = 2$$

$$B = ? \quad C = ?$$

$$2(s^2 + 4s + 13) + Bs^2 + Cs = 26$$

$$(2+B)s^2 + (8+C)s = 0$$

$$B = -2, \quad C = -8$$

$$\therefore V(s) = \frac{2}{s} + \frac{-2s - 8}{s^2 + 4s + 13}$$

$$= \frac{2}{s} + \frac{-2s - 8}{(s+2)^2 + 3^2}$$

$$= \frac{2}{s} + \frac{-2(s+2)}{(s+2)^2 + 3^2} + \frac{\frac{-4}{3} \times 3}{(s+2)^2 + 3^2}$$

$$\xrightarrow{\mathcal{L}^{-1}} v(t) = 2 - 2e^{-2t} \cos 3t - \frac{4}{3}e^{-2t} \sin 3t, t \geq 0.$$

$$\textcircled{28} \ddot{v}(t) + 9v(t) = 9u_s(t), v(0) = \dot{v}(0) = 0$$

$$\xrightarrow{\mathcal{L}} s^2 V(s) + 9V(s) = \frac{9}{s}$$

$$V(s) = \frac{9}{s(s^2 + 9)}$$

$$= \frac{A}{s} + \frac{Bs + C}{s^2 + 9}$$

$$A = \frac{9}{s(s^2 + 9)} \times s \Big|_{s=0} = 1$$

$$B = ? \quad C = ?$$

$$s^2 + 9 + Bs^2 + Cs = 9$$


$$(1+B)s^2 + Cs = 0$$

$$B = -1, \quad C = 0.$$

$$\therefore V(s) = \frac{1}{s} + \frac{-s}{s^2 + 3^2}$$

$$\xrightarrow{\mathcal{L}^{-1}} v(t) = 1 - \cos 3t, t \geq 0$$

$$* \textcircled{29} v(3)$$

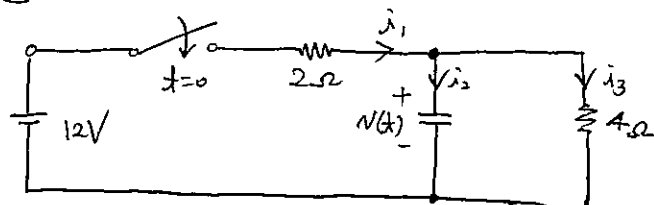


$$\textcircled{29} t = 0^- \text{ or } 4$$

$$i_1(0^-) = i_2(0^-) = i_3(0^-) = 0 [A]$$

$$v(0^-) = 0 [V]$$

② $t=0^+$ 때

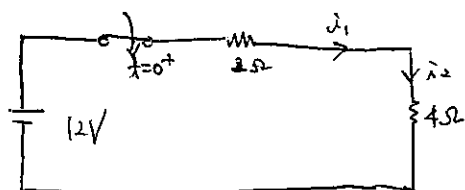


$$i_1(0^+) = i_2(0^+) = \frac{12}{2} = 6 \text{ [A]}$$

$$i_3(0^+) = 0 \text{ [A]}$$

$$v_L(0^-) = v_L(0^+) = 0 \text{ [V]}$$

③ $t=\infty$ 때

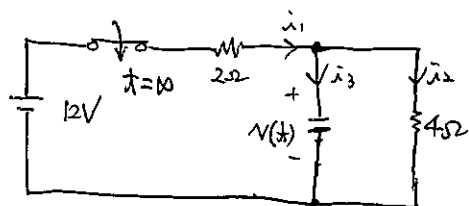


$$i_1(\infty) = i_3(\infty) = \frac{12}{2+4} = 2 \text{ [A]}$$


$$i_2(\infty) = 0 \text{ [A]}$$

$$v_L(\infty) = 12 \times \frac{4}{2+4} = 8 \text{ [V]}$$

* ② ~ ④

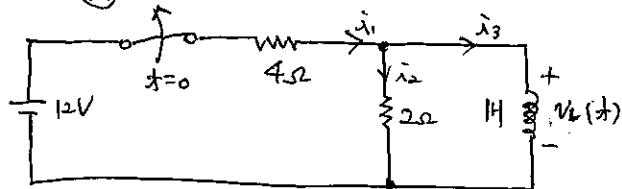

② $t=0^-$ 때

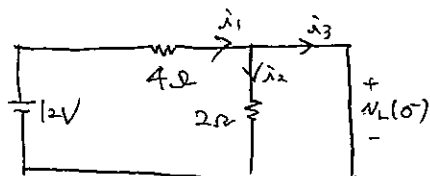


$$i_1(0^-) = i_3(0^-) = \frac{12}{4} = 3 \text{ [A]}$$

$$i_2(0^-) = 0 \text{ [A]}$$

$$v_L(0^-) = 0 \text{ [V]}$$

③ $t=0^+$ 때

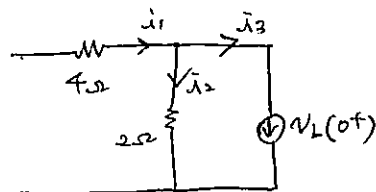


$$i_1(0^+) = 0 \text{ [A]}$$

$$i_3(0^+) = i_3(0^-) = 3 \text{ [A]}$$

$$i_2(0^+) = -3 \text{ [A]}$$

$$v_L(0^+) = -3 \times 2 = -6 \text{ [V]}$$


④ $t=\infty$ 때

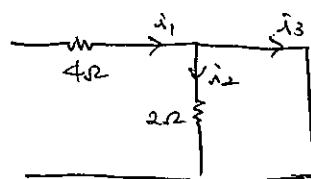

$$i_1(\infty) = i_2(\infty) = i_3(\infty) = 0 \text{ [A]}$$

$$v_L(\infty) = 0 \text{ [V]}$$

* ⑤ ~ ⑨

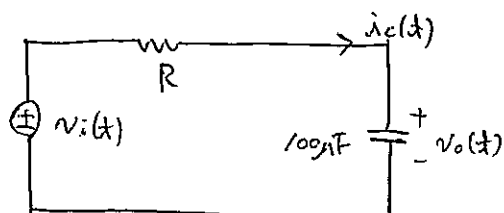

⑤ v_i 와 v_o 관계식

$$v_i(t) = R \cdot i_c(t) + v_o(t)$$

$$* i_c(t) = 100 \mu\text{F} \cdot \frac{d v_o(t)}{dt}$$

$$\therefore v_i(t) = R \cdot 100 \mu\text{F} \cdot \frac{d v_o(t)}{dt} + v_o(t)$$

⑥ 선형임을 보이기

* 비례성과 중첩성을 만족해야 선형

1) 비례성

$$\alpha v_i(t) = \alpha (R \cdot 100 \mu\text{F} \cdot \frac{d v_o(t)}{dt} + v_o(t))$$

$$= R \cdot 100 \mu\text{F} \cdot \frac{d}{dt} \alpha v_o(t) + \alpha v_o(t)$$

- 7 - $\alpha v_i(t)$ 에 대한 $\alpha v_o(t)$ 성립 $\Rightarrow$ 비례성

ii) 중첩성

입력을 $v_i = v_{i1} + v_{i2}$ 일 때

$$v_{i1} = R \cdot 100\mu \cdot \frac{d}{dt} v_{o1}(t) + v_{o1}(t)$$

$$v_{i2} = R \cdot 100\mu \cdot \frac{d}{dt} v_{o2}(t) + v_{o2}(t)$$

$$\Rightarrow v_{i1} + v_{i2} = R \cdot 100\mu \cdot \frac{d}{dt} (v_{o1}(t) + v_{o2}(t)) + (v_{o1}(t) + v_{o2}(t))$$

가 성립. $\Rightarrow$ 중첩성.

즉, 중첩성과 비례성 모두 만족하므로 선형.

㉓) 시간상

$$\tau = RC$$

$$\tau = R \times 100\mu$$

$$= R \times 100 \times 10^{-6} = R \times 10^{-4} [s]$$

㉔). ㉓) $v_o(t)$ 파형 그리기

정상상태 정상상태 시간.


정상상태 (5 τ 일 때)

$$R=1k\Omega \rightarrow \tau=0.1s, 5\tau=0.5s$$


$$R=2k\Omega \rightarrow \tau=0.2s, 5\tau=1s$$

$$R=10k\Omega \rightarrow \tau=1s, 5\tau=5s$$
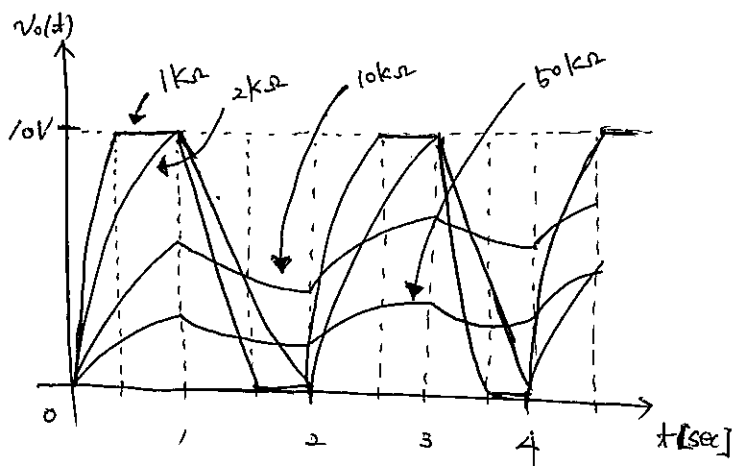
$$R=50k\Omega \rightarrow \tau=5s, 5\tau=25s$$




* ㉕) ~ ㉗)

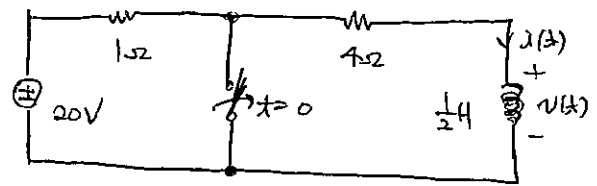

㉕) ㉕)


i) $t=0^-$ 일 때

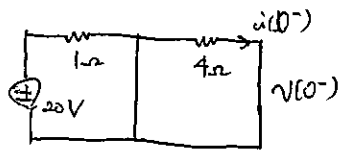

$$i(0^-) = 0 [A]$$

$$v(0^-) = 0 [V]$$


ii) $t=0^+$ 일 때

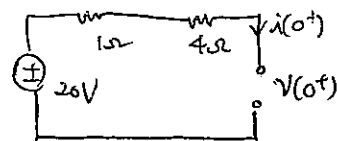

$$i(0^+) = i(0^-) = 0 [A]$$

$$v(0^+) = 20 [V]$$

iii) $t > 0$

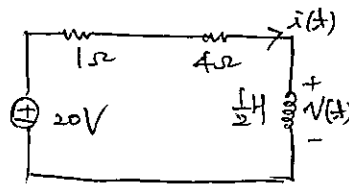

$$20 = 5i(t) + v(t)$$

$$* \boxed{v(t) = L \cdot \frac{di(t)}{dt}} \text{ 이라 하자.}$$

$$v(t) = \frac{1}{2} \cdot \frac{d}{dt} i(t)$$

$$20 = 5i(t) + \frac{1}{2} \cdot \frac{d}{dt} i(t)$$

$$40 = 10i(t) + \frac{d}{dt} i(t)$$

$$\xrightarrow{L} sI(s) + 10I(s) = \frac{40}{s} \quad (\because i(0) = 0 \text{ 이라 하자})$$

$$I(s) = \frac{40}{s(s+10)}$$

$$= \frac{A}{s} + \frac{B}{s+10}$$

$$A = \frac{40}{s(s+10)} \times s \Big|_{s=0} = 4$$

$$B = \frac{40}{s(s+10)} \times (s+10) \Big|_{s=-10} = -4$$

$$\therefore I(s) = \frac{4}{s} + \frac{-4}{s+10}$$



$$\xrightarrow{\mathcal{L}^{-1}} i(t) = 4 - 4e^{-10t} \text{ [A]}, t \geq 0$$

$$\text{또한, } v(t) = H \cdot \frac{d}{dt} i(t) \text{ 이므로}$$

$$= \frac{1}{2} \times \frac{d}{dt} (4 - 4e^{-10t})$$

$$v(t) = 20e^{-10t} \text{ [V]}, t \geq 0$$


graph. (43)

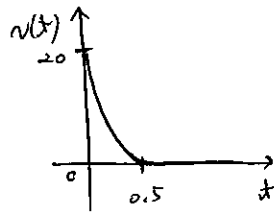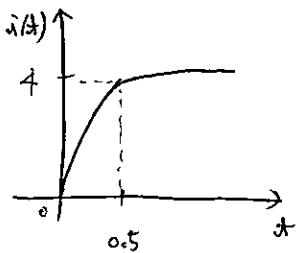


④2 $t > 0$ 일 때 스위치

$$\tau = \frac{L}{R} = \frac{\frac{1}{2}}{5} = \frac{1}{10} = 0.1 \text{ [sec]}$$

* ④3 ~ ④8

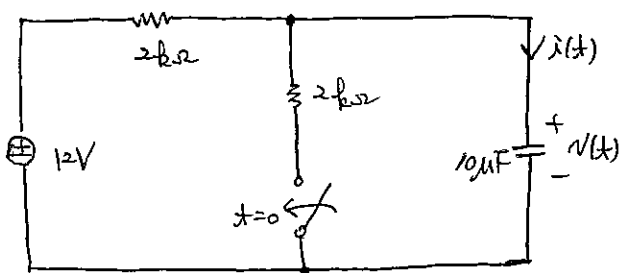


④3 $t > 0^-$ 일 때

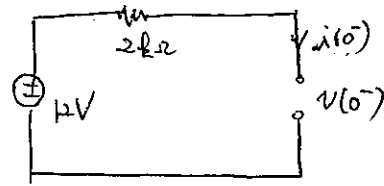

$$i(0^-) = 0 \text{ [A]} \quad v(0^-) = 12 \text{ [V]}$$

④4 $t = 0^+$ 일 때

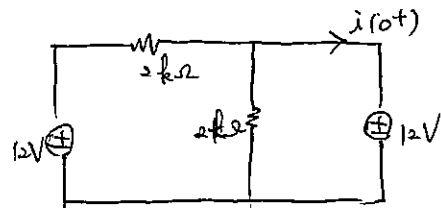

$$v(0^+) = v(0^-) = 12 \text{ [V]}$$


$$i(0^+) = \frac{-12}{2k} = -6 \text{ [mA]}$$

④5 $t > 0$ 일 때

테브난의 등가회로 바꾸면

$$R_{TH} = 2k\Omega // 2k\Omega = 1k\Omega$$
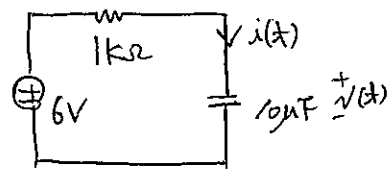
$$V_{OC} = 12 \times \frac{2k}{2k+2k} = 6 \text{ V}$$



$$6 = 1k \cdot i(t) + v(t)$$

$$\star \left[i(t) = C \cdot \frac{dv(t)}{dt} \right] \text{ 이므로}$$

$$i(t) = 10\mu \cdot \frac{dv(t)}{dt}$$

$$6 = 1k \cdot 10\mu \cdot \frac{dv(t)}{dt} + v(t)$$

$$600 = \frac{dv(t)}{dt} + 100 v(t)$$

$$\rightarrow sV(s) - v(0^+) + 100V(s) = \frac{600}{s}$$

$$(v(0^+) = 12[V] \text{ 이므로})$$

$$(s+100)V(s) = \frac{600}{s} + 12$$

$$V(s) = \frac{12s + 600}{s(s+100)}$$

$$= \frac{A}{s} + \frac{B}{s+100}$$

$$A = \frac{12s+600}{s(s+100)} \times s \Big|_{s=0} = 6$$

$$B = \frac{12s+600}{s(s+100)} \times (s+100) \Big|_{s=-100} = 6$$

$$\therefore V(s) = \frac{6}{s} + \frac{6}{s+100}$$

$$\xrightarrow{\mathcal{P}^{-1}} v(t) = 6 + 6e^{-100t} [V], t \geq 0$$

$$i(t) = C \cdot \frac{d}{dt} v(t) \text{ 이므로}$$

$$= 10\mu \cdot \frac{d}{dt} (6 + 6e^{-100t})$$

$$i(t) = -6e^{-100t} [mA], t \geq 0$$

$$\textcircled{45} v(\infty) = \lim_{t \rightarrow \infty} (6 + 6e^{-100t}) = 6 [V]$$

$$i(\infty) = \lim_{t \rightarrow \infty} (-6e^{-100t}) = 0 [A]$$

$$\textcircled{46} v(t) = 6 + 6 \cdot e^{-100t} [V], t \geq 0$$

$$i(t) = -6e^{-100t} [mA], t \geq 0$$



$\textcircled{47} t > 0$ 에서 정상상태 시간

$$\tau = R \cdot C = 1k\Omega \times 10\mu F$$

$$= 0.01 [s]$$

정상상태 시간 $\tau = 0.05 [s]$ 에서 정상상태 도달
시간 -10-

$\textcircled{48} v(t), i(t)$ 파형 graph

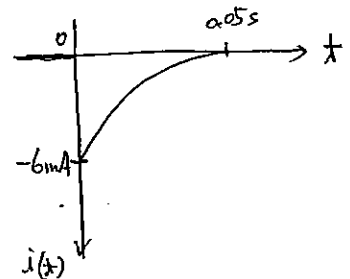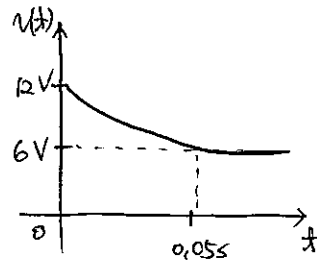

수고했습니다. 좋은 결과 있으시길 ... ^^