

2018년 2학기 기말

20181229 최현서

(회로이론)

1




$10 \times 10^4 \text{ PF}$

$\pm 5\%$



오차 $\pm 5\%$ $\pm 10\%$ $\pm 20\%$
J K M

2.

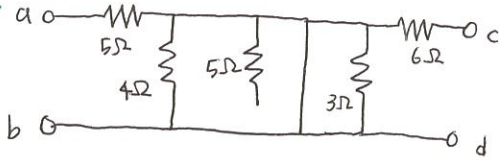


$$R_{ab} = 5\Omega$$

$$R_{cd} = 6\Omega$$

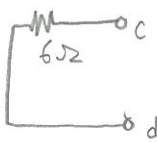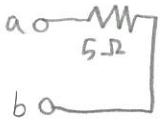


3.

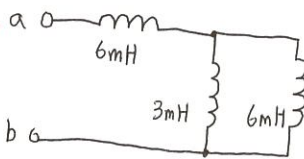

병렬 연결 $3\text{mH}, 6\text{mH} \Rightarrow \frac{3 \times 6}{3+6} = 2\text{mH}$

$$L_{eq} = 6 + 2 = 8\text{mH}$$


4.

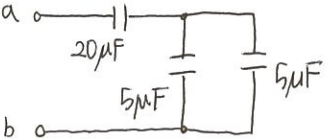

병렬 연결 $5\mu\text{F} + 5\mu\text{F} = 10\mu\text{F}$

$$C_{eq} = \frac{20 \times 10}{20 + 10} = \frac{20}{3} \mu\text{F}$$

5~8

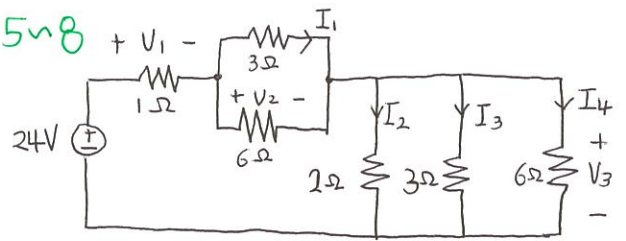

$$5. \quad 3//6 = 2\Omega \quad 2//3//6 = 1\Omega$$

$$I_a = \frac{24}{1+2+1} = \frac{24}{4} = 6\text{A}$$

$$I_1 = I_a \times \frac{6}{3+6} = 6 \times \frac{2}{3} = 4\text{A}$$

$$I_2 = I_a \times \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{3} + \frac{1}{6}} = 6 \times \frac{\frac{1}{2}}{1} = 3\text{A}$$

$$I_3 = I_a \times \frac{\frac{1}{3}}{\frac{1}{2} + \frac{1}{3} + \frac{1}{6}} = 6 \times \frac{\frac{1}{3}}{1} = 2\text{A}$$

$$I_4 = I_a \times \frac{\frac{1}{6}}{\frac{1}{2} + \frac{1}{3} + \frac{1}{6}} = 6 \times \frac{\frac{1}{6}}{1} = 1\text{A}$$

$$6. \quad V_1 = 1 \times I_a = 6\text{V}$$

$$V_2 = 3 \times I_1 = 12\text{V}$$


$$V_3 = 2I_2 = 3I_3 = 6I_4 = 6\text{V}$$

$$7. \quad P_{1\Omega} = V \cdot I = 6 \times 6 = 36 \text{ watt/t}$$



$$8. \quad W = \int_0^{10} P_{1\Omega} dt$$

$$= 36 \int_0^{10} dt = 360\text{J}$$

9~10

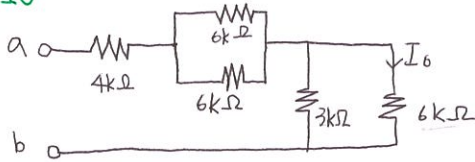


9.

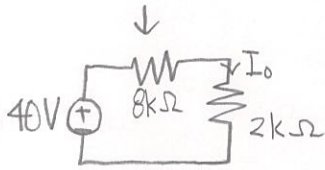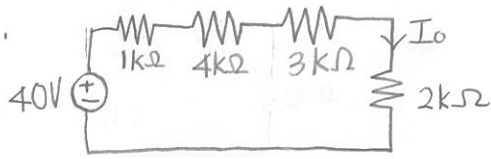

$$I = \frac{40V}{10k\Omega} = 4mA$$

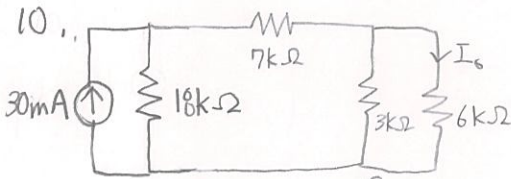
$$I_0 = \frac{3}{3+6} \times 4 = \frac{1}{3} \times 4 = \frac{4}{3}mA$$




$$I = \frac{18}{18+7+2} \times 30 = 20mA$$

$$I_0 = I \times \frac{3}{3+6} = 20 \times \frac{3}{9} = \frac{20}{3}mA$$

11~13

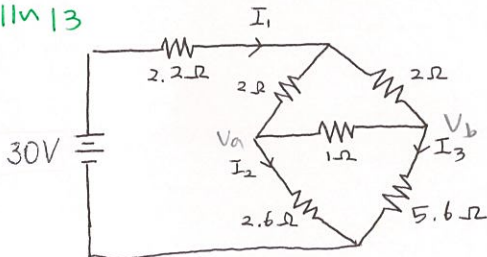

11. Req

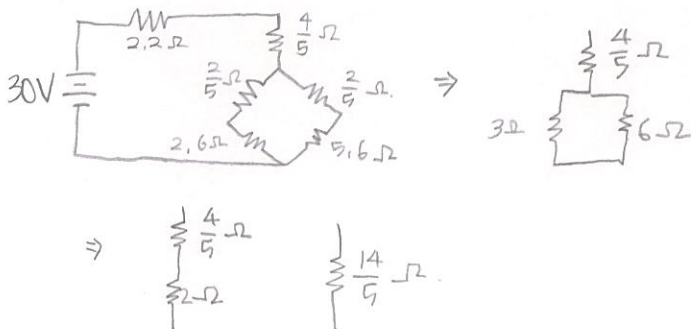

$$Req = 2.2 + 2.8 = 5\Omega$$

$$12. I_1 = \frac{30}{5} = 6[A]$$

$$I_2 = \frac{6}{3+6} \times I_1 = \frac{2}{3} \times 6 = 4A$$

$$I_3 = \frac{3}{3+6} \times I_1 = \frac{1}{3} \times 6 = 2A$$


13.

$$V_a = 2.6 \times I_2 = 10.4V$$

$$V_b = 5.6 \times I_3 = 11.2V$$

$$I_4 = \frac{V_a - V_b}{1} = -0.8A$$

14~18

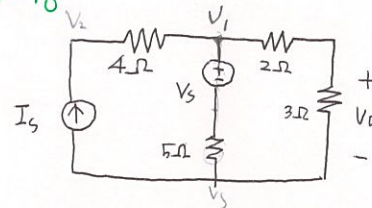

$$14. \frac{V_0}{3} + \frac{V_0 - V_1}{2} = 0$$

$$5V_0 = 3V_1 \dots ①$$

V_1 에서 KCL 적용

$$I_s = \frac{V_1 - V_s}{5} + \frac{V_1}{5}$$

$$5I_s = 2V_1 - V_s$$

$$5I_s + V_s = 2V_1$$

$$\frac{10}{3}V_0 = 5I_s + V_s$$

$$V_0 = \frac{3}{2}I_s + \frac{3}{10}V_s$$




$$5(I_1 - I_s) + 2I_1 + 3I_1 - V_s = 0$$

$$V_s = 10I_1 - 5I_s$$

$$3I_1 = V_o$$

$$V_s = \frac{10}{3}V_o - 5I_s$$
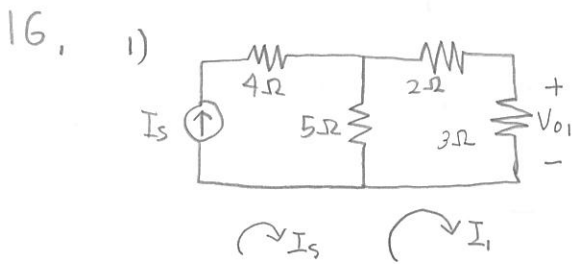
$$V_o = \frac{3}{10}V_s + \frac{3}{2}I_s$$




$$5(I_1 - I_s) + 2I_1 + 3I_1 = 0$$

$$10I_1 = 5I_s \quad \dots ①$$

$$V_{o1} = 3I_1$$

$$\frac{10}{3}V_{o1} = 5I_s$$

$$V_{o1} = \frac{3}{2}I_s$$

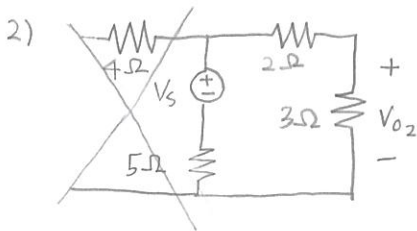


$$V_{o2} = \frac{3}{10}V_s$$

$$V_o = V_{o1} + V_{o2} = \frac{3}{10}V_s + \frac{3}{2}I_s$$



$$R_{TH} = 7\Omega$$

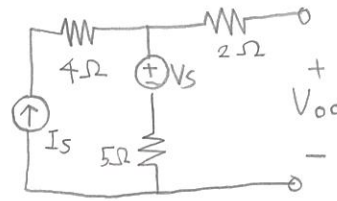


$$I_s = \frac{V_{oc} - V_s}{5}$$

$$5I_s = V_{oc} - V_s$$


$$V_{oc} = V_s + 5I_s$$

<테빈안 등가회로>

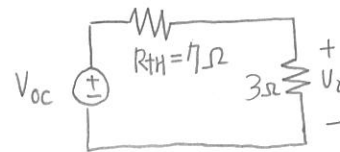

$$V_o = \frac{3}{10}V_{oc} = \frac{3}{10}(V_s + 5I_s)$$

$$= \frac{3}{10}V_s + \frac{3}{2}I_s$$

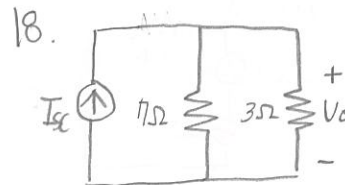


$$I_{sc} = \frac{V_{oc}}{R_{TH}} = \frac{V_s + 5I_s}{7}$$

$$V_o = (7//3)I_{sc}$$

$$= \frac{21}{10}\left(\frac{1}{7}V_s + \frac{5}{7}I_s\right)$$

$$= \frac{3}{10}V_s + \frac{3}{2}I_s$$

19, 23

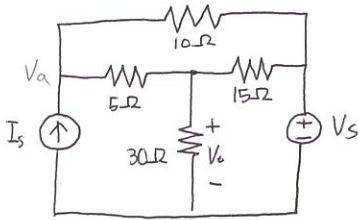

19.

$$\textcircled{1} \frac{V_s - V_0}{15} + \frac{V_a - V_0}{5} = \frac{V_0}{30}$$

$$2V_s - 2V_0 + 6V_a - 6V_0 = V_0$$

$$9V_0 = 2V_s + 6V_a$$

$$\textcircled{2} I_s = \frac{V_a - V_0}{5} + \frac{V_a - V_s}{10}$$

$$10I_s = 2V_a - 2V_0 + V_a - V_s$$

$$2V_0 = -10I_s + 3V_a - V_s$$


$$\Rightarrow 9V_0 = 2V_s + 6V_a$$

$$- \quad 4V_0 = 2V_s + 6V_a - 20I_s$$

$$5V_0 = 4V_s + 20I_s$$

$$V_0 = \frac{4}{5}V_s + 4I_s$$

20.

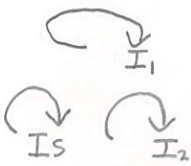

$$\begin{aligned} I_1 \text{ KVL} \Rightarrow \textcircled{1} & 10I_1 + 5(I_1 - I_s) + 15(I_1 - I_2) = 0 \\ & 30I_1 - 15I_2 = 5I_s \quad \dots \textcircled{1} \end{aligned}$$

$$\begin{aligned} I_2 \text{ KVL} \Rightarrow \textcircled{2} & V_s + 15(I_2 - I_1) + 30(I_2 - I_s) = 0 \\ & V_s + 45I_2 - 15I_1 - 30I_s = 0 \\ & -15I_1 + 45I_2 = -V_s + 30I_s \quad \dots \textcircled{2} \end{aligned}$$

$$\star V_0 = 30(I_s - I_2)$$

$$\Rightarrow \textcircled{1} + \textcircled{2} \times 2 \quad 30I_1 - 15I_2 = 5I_s$$


$$+ \quad -30I_1 + 90I_2 = 60I_s - 2V_s$$

$$75I_2 = -2V_s + 65I_s$$

$$I_2 = -\frac{2}{75}V_s + \frac{13}{15}I_s$$


$$\Rightarrow V_0 = 4I_s + \frac{4}{5}V_s$$

21.

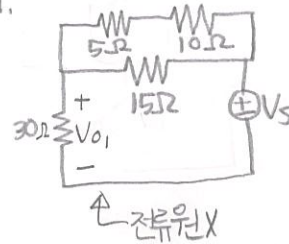

$$\rightarrow V_{01} = V_s \times \frac{30}{30 + \frac{15}{2}}$$

$$V_{01} = \frac{4}{5}V_s$$

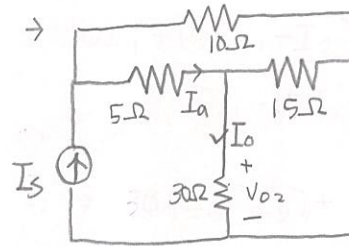

$$\star V_{02} = 30I_0$$


$$I_a = I_s \times \frac{10}{10 + (5 + 30 \parallel 15)} = \frac{2}{5}I_s$$

$$I_0 = I_a \times \frac{15}{30 + 15} = \frac{2}{5}I_s \times \frac{1}{3} = \frac{2}{15}I_s$$


$$V_{02} = 30 \cdot \frac{2}{15}I_s = 4I_s$$

$$V_0 = V_{01} + V_{02} = \frac{4}{5}V_s + 4I_s$$

22.

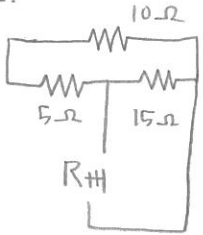
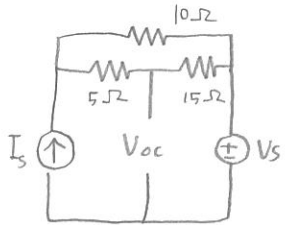
$$R_{TH} = (10 + 5) // 15 \\ = 7.5 \Omega$$



중첩의 원리


$$V_{oc} = V_s + 5I_s$$



$$V_o = (V_s + 5I_s) \times \frac{30}{30 + 7.5}$$

$$= \frac{4}{5} V_s + 4I_s$$

23.

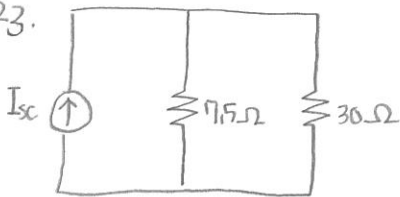


$$I_{sc} = \frac{V_{oc}}{R_{TH}} = \frac{V_s + 5I_s}{7.5} = \frac{2}{15} V_s + \frac{2}{3} I_s$$

$$V_o = (7.5 // 30) I_{sc}$$

$$= 6 I_{sc}$$

$$V_o = 6 \left(\frac{2}{15} V_s + \frac{2}{3} I_s \right) = \frac{4}{5} V_s + 4I_s$$

24 ~ 25

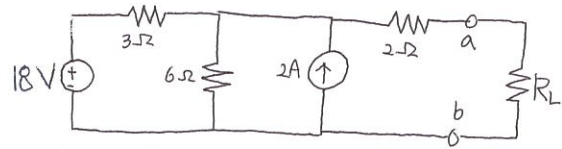

$$24. R_{eq} = 2 + (3 // 6) = 4 \Omega$$

$$V_{oc} = 18 \times \frac{6}{3+6} + 6 \times 2 \times \frac{3}{3+6} = 16V$$




$$R_L = R_{eq} = 4$$

$$25. P_{L, max} = R_{eq} \times \left(\frac{V_{oc}}{2R_{eq}} \right)^2 = \frac{V_{oc}^2}{4R_{eq}}$$


$$= \frac{16 \cdot 16}{4 \cdot 4} = 16W$$

26 ~ 29

(FET 모델)

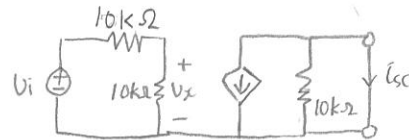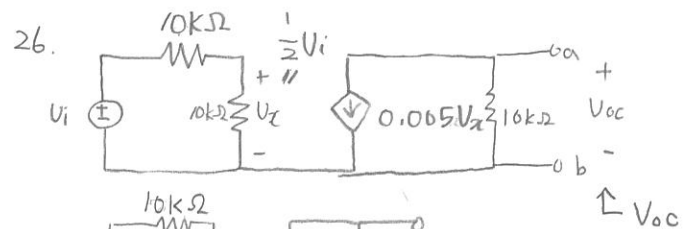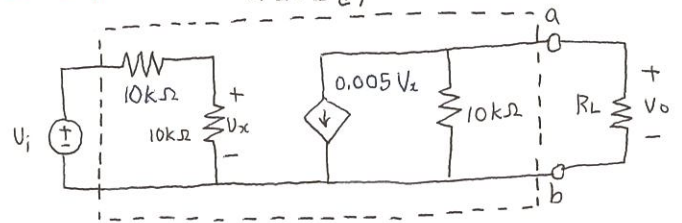

← Isc

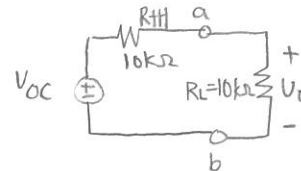

$$V_{oc} = -10 \times 10^3 \times 0.005 V_x = -50 V_x$$

$$V_x = \frac{1}{2} V_i$$

$$V_{oc} = -25 V_i$$

$$I_{sc} = -0.005 V_x$$

$$= -0.0025 V_i$$

$$R_{eq} = \frac{V_{oc}}{I_{sc}} = \frac{-25 V_i}{-0.0025 V_i} = 10 k\Omega$$

$$27. R_{eq} = R_L \leftarrow \text{최대}$$

$$R_{eq} = 10k\Omega$$


$$28. P_{L,max} = \frac{V_{oc}^2}{4R_{eq}} = \frac{(-25V_i)^2}{4 \cdot 10} = \frac{625V_i^2}{40}$$

$$= 15.6 V_i^2 [mW]$$

$$29. V_o = \frac{10}{10+10} V_{oc} = \frac{1}{2} V_{oc} = -\frac{25}{2} V_i$$

$$\text{전압이득} \quad \frac{V_o}{V_i} = -\frac{25}{2}$$

30.

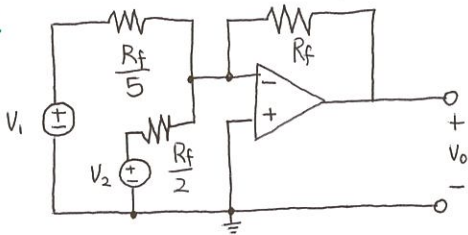


$$\frac{V_1 - 0}{\frac{R_f}{5}} + \frac{V_2 - 0}{\frac{R_f}{2}} + \frac{V_0 - 0}{R_f} = 0$$

$$5V_1 + 2V_2 + V_0 = 0$$

$$V_0 = -(5V_1 + 2V_2)$$

31.

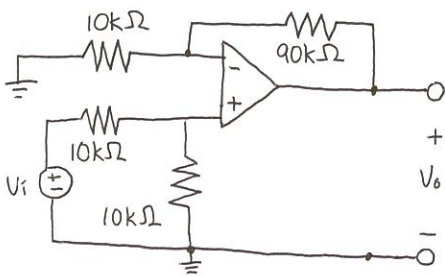

반전단자 $\Rightarrow$ KCL 적용

$$\frac{0 - V_-}{10k} + \frac{V_0 - V_-}{90k} = 0$$

$$-9V_- + V_0 - V_- = 0$$

$$V_- = \frac{1}{10} V_0$$

비반전단자 $\Rightarrow$ KCL 적용

$$\frac{V_i - V_+}{10} + \frac{0 - V_+}{10} = 0$$

$$V_i - V_+ - V_+ = 0$$

$$V_+ = \frac{1}{2} V_i$$

$$V_- = V_+$$

$$\frac{1}{10} V_0 = \frac{1}{2} V_i \quad V_0 = 5V_i$$

$$\text{전압이득} \Rightarrow \frac{V_o}{V_i} = \frac{5V_i}{V_i} = 5$$

32~36 2차미분방정식의 해 $x(t), t \geq 0$ 라플라스 변환

$$32. \frac{d^2v(t)}{dt^2} + 3 \frac{dv(t)}{dt} + 2v(t) = 8, v(0)=2, \dot{v}=0$$

$$\{s^2V(s) - sV(0) - \dot{V}(0)\} + 3\{sV(s) - V(0)\} + 2V(s) = \frac{8}{s}$$

$$(s^2 + 3s + 2)V(s) - sV(0) - 3V(0) - \dot{V}(0) = \frac{8}{s}$$

$$V(s) = \frac{8}{s(s+1)(s+2)} + \frac{2(s+3)}{(s+1)(s+2)}$$

$$= \frac{2(s^2 + 3s + 4)}{s(s+1)(s+2)} = \frac{2s^2 + 6s + 8}{s(s+1)(s+2)}$$

$$k_1 = \{V(s)s\}|_{s=0}$$

$$= \frac{2s^2 + 6s + 8}{(s+1)(s+2)} \Big|_{s=0} = \frac{8}{2} = 4$$

$$k_2 = \{V(s)(s+1)\}|_{s=-1}$$

$$= \frac{2s^2 + 6s + 8}{s(s+2)} \Big|_{s=-1} = \frac{2-6+8}{-1} = -4$$

$$k_3 = \{V(s)(s+2)\}|_{s=-2}$$

$$= \frac{2s^2 + 6s + 8}{s(s+1)} \Big|_{s=-2} = \frac{8-12+8}{2} = \frac{4}{2} = 2$$

$$V(s) = \frac{4}{s} + \frac{-4}{s+1} + \frac{2}{s+2}$$

$$v(t) = 4 - 4e^{-t} + 2e^{-2t}$$

$$33. \frac{d^2 v(t)}{dt^2} + 5 \frac{dv(t)}{dt} + 6v(t) = 24 \cos 3t$$

$$\{s^2 V(s) - s v(0) - \dot{v}(0)\} + 5 \{s V(s) - v(0)\} + 6 V(s) = \frac{24s}{s^2 + 9}$$

$$(s^2 + 5s + 6) V(s) = \frac{24s}{s^2 + 9}$$

$$V(s) = \frac{24s}{(s^2 + 9)(s+3)(s+2)}$$

$$= \frac{C_1 s + C_2}{s^2 + 9} + \frac{k_1}{s+3} + \frac{k_2}{s+2}$$

$$k_1 = (s+2) V(s) \big|_{s=-2}$$

$$= \frac{24s}{(s+3)(s^2+9)} \big|_{s=-2}$$

$$= -\frac{48}{13}$$

$$k_2 = (s+3) V(s) \big|_{s=-3}$$

$$= \frac{24s}{(s+2)(s^2+9)} \big|_{s=-3}$$

$$= \frac{8}{2} = 4$$

$$24s = -\frac{48}{13} (s+3)(s^2+9) + 4(s+2)(s^2+9) + (C_1 s + C_2)(s+2)(s+3)$$

$$= \left(-\frac{48}{13} + 4 + C_1\right) s^3 + \left(-\frac{48}{13} + 3 + 8 + 5C_1 + C_2\right) s^2 + \left(-\frac{48}{13} \times 9 + 36 + 6C_1 + 5C_2\right) s + \left(-\frac{48}{13} \times 27 + 4 \times 18 + 6C_2\right)$$

$$-\frac{48}{13} + 4 + C_1 = 0 \quad C_1 = -\frac{4}{13}$$

$$-\frac{48}{13} \times 3 + 8 + 5C_1 + C_2 = 0 \quad C_2 = \frac{60}{13}$$

$$V(s) = \frac{-\frac{4}{13}s + \frac{60}{13}}{s^2 + 9} + \frac{4}{s+3} + \frac{-\frac{48}{13}}{s+2}$$

$$v(t) = -\frac{48}{13} e^{-2t} + 4e^{-3t} - \frac{4}{13} \cos 3t + \frac{20}{13} \sin 3t$$

$$34. \frac{d^2 v(t)}{dt^2} + 2 \frac{dv(t)}{dt} + v(t) = 8, \quad v(0) = \dot{v}(0) = 0$$

$$\{s^2 V(s) - s v(0) - \dot{v}(0)\} + 2 \{s V(s) - v(0)\} + V(s) = \frac{8}{s}$$

$$(s^2 + 2s + 1) V(s) = \frac{8}{s}$$

$$V(s) = \frac{8}{s(s+1)^2}$$

$$= \frac{k_1}{s} + \frac{k_2}{(s+1)^2} + \frac{k_3}{s+1}$$

$$k_1 = \{V(s)s\} \big|_{s=0}$$

$$= \frac{8}{(s+1)^2} \big|_{s=0} = 8$$

$$k_2 = \{V(s)(s+1)^2\} \big|_{s=-1}$$

$$= \frac{8}{s} \big|_{s=-1} = -8$$

$$k_3 = \left[\frac{d}{ds} \{V(s)(s+1)^2\} \right] \big|_{s=-1}$$

$$= \frac{-8}{s^2} \big|_{s=-1} = -8$$

$$V(s) = \frac{8}{s} + \frac{-8}{(s+1)^2} + \frac{-8}{s+1}$$

$$v(t) = 8 - 8te^{-t} - 8e^{-t}$$

$$35. \frac{d^2 v(t)}{dt^2} + 4v(t) = 16, \quad v(0) = \dot{v}(0) = 0$$

$$\{s^2 V(s) - s v(0) - \dot{v}(0)\} + 4V(s) = \frac{16}{s}$$

$$(s^2 + 4)V(s) = \frac{16}{s}$$

$$V(s) = \frac{16}{s(s^2 + 4)}$$

$$= \frac{k_1}{s} + \frac{c_1 s + c_2}{s^2 + 4}$$

$$(k_1 + c_1)s^2 = 0$$

$$c_2 s = 0$$

$$4k_1 = 16$$

$$\Rightarrow k_1 = 4$$

$$c_1 = -4$$

$$V(s) = \frac{4}{s} + \frac{-4s}{s^2 + 4}$$

$$v(t) = 4 - 4\cos 2t, \quad t \geq 0$$

$$36. \frac{d^2 v(t)}{dt^2} + 2 \frac{dv(t)}{dt} + 2v(t) = 8u_s(t), \quad v(0) = \dot{v}(0) = 0$$

$$\{s^2 V(s) - s v(0) - \dot{v}(0)\} + 2\{s V(s) - v(0)\} + 2V(s) = \frac{8}{s}$$

$$(s^2 + 2s + 2)V(s) = \frac{8}{s}$$

$$V(s) = \frac{8}{s(s^2 + 2s + 2)}$$

$$= \frac{k_1}{s} + \frac{c_1 s + c_2}{s^2 + 2s + 2}$$

$$(k_1 + c_1)s^2 = 0$$

$$(2k_1 + c_2)s = 0$$

$$2k_1 = 8$$

$$\Rightarrow k_1 = 4$$

$$c_1 = -4$$


$$c_2 = -8$$

$$V(s) = \frac{4}{s} + \frac{-4s - 8}{s^2 + 2s + 2} = \frac{4}{s} + \frac{-4(s+1) - 4}{(s+1)^2 + 1^2}$$

$$v(t) = 4 - 4e^{-t} \cos t - 4e^{-t} \sin t$$

$$= 4 - 4e^{-t}(\cos t + \sin t), \quad t \geq 0$$

37 ~ 39

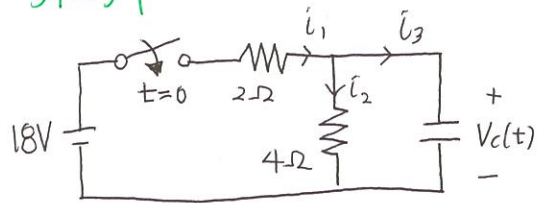


37. $t = 0^-$ 시점의 $V_c, \hat{i}_1, \hat{i}_2, \hat{i}_3$

$$\hat{i}_1(0^-) = \hat{i}_2(0^-) = \hat{i}_3(0^-) = 0 \text{ [A]}$$

$$V_c(0^-) = 0 \text{ [V]}$$

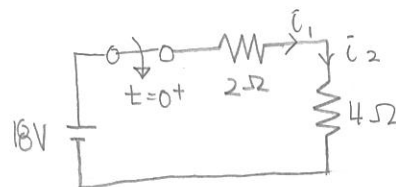38. $t = 0^+$ 시점의 $V_c, \hat{i}_1, \hat{i}_2, \hat{i}_3$




$$V_c(0^+) = V_c(0^-) = 0 \text{ [V]}$$

$$\hat{i}_2(0^+) = \frac{V_c(0^+)}{4} = 0 \text{ [A]}$$

$$\hat{i}_1(0^+) = \frac{18 - 0}{2} = 9 \text{ [A]}$$
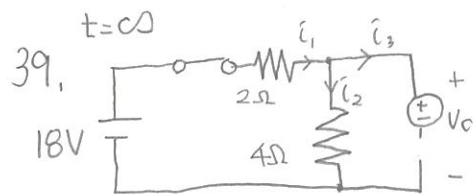
$$\hat{i}_3 = \hat{i}_1 = 9 \text{ [A]}$$





$$V_c(\infty) = 18 \times \frac{4}{2+4} = 12 \text{ [V]}$$

$$\hat{i}_1(\infty) = \hat{i}_2(\infty) = \frac{18}{6} = 3 \text{ [A]}$$

$$\hat{i}_3(\infty) = 0 \text{ [A]}$$

40~42

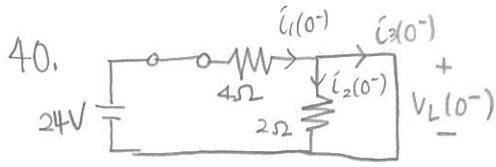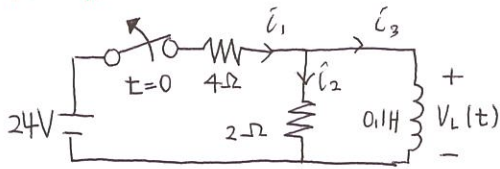


$t=0^-$

$V_L(0^-) = 0 [V] \leftarrow$ 일정한 전류 흘러서

$$i_1(0^-) = \frac{24}{4} = 6 [A]$$

$$i_3(0^-) = i_1(0^-) = 6 [A]$$

$$i_2(0^-) = 0 A$$

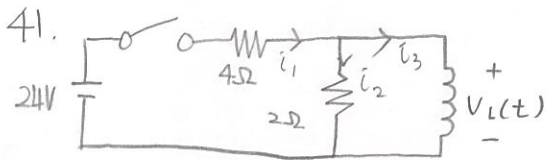

$$i_3(0^+) = i_3(0^-) = 6 [A]$$

$$i_2 = -i_3(0^+) = -6 [A]$$

$$i_1(0^+) = 0 [A]$$


$$V_L(0^+) = 2 \times i_2(0^+) = -12 [V]$$

42. 시간이 지남에 따라 0J

$$V_L(t) = 0 [V]$$

$$i_1(\infty) = i_2(\infty) = i_3(\infty) = 0 [A]$$

43~47

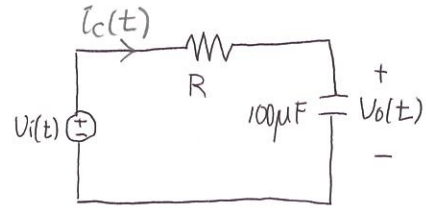

$$43. V_i(t) = i_C(t)R + V_o(t)$$

$$i_C(t) = 100\mu F \cdot \frac{dV_o(t)}{dt}$$

$$V_i(t) = 100\mu F \cdot R \cdot \frac{dV_o(t)}{dt} + V_o(t)$$

44. 1) 입력이 $\partial V_i(t)$ 일때,

$$\partial V_i(t) = \partial \left(100\mu F \cdot R \cdot \frac{dV_o(t)}{dt} + V_o(t) \right)$$

$$= 100\mu F \cdot R \cdot \frac{d}{dt} \partial V_o(t) + \partial V_o(t)$$

출력 $\partial V_o(t)$ 성립 $\leftarrow$ 비례성 만족

2) 입력 $V_{i1}(t) + V_{i2}(t)$ 일때,

$$V_{i1}(t) = 100\mu F \cdot R \cdot \frac{d}{dt} V_{o1}(t) + V_{o1}(t)$$

$$V_{i2}(t) = 100\mu F \cdot R \cdot \frac{d}{dt} V_{o2}(t) + V_{o2}(t)$$

$$V_{i1}(t) + V_{i2}(t) = 100\mu F \cdot R \cdot \frac{d}{dt} (V_{o1}(t) + V_{o2}(t)) + (V_{o1}(t) + V_{o2}(t))$$

출력 $V_{o1}(t) + V_{o2}(t)$ 성립 $\leftarrow$ 중첩성 만족

$\Rightarrow$ 비례성, 중첩성을 만족시키므로 선형이다.

$$45. \tau = RC$$

$$= R \times 100 \times 10^{-6} = R \times 10^{-4} [s]$$


46 ~ 47

$$R = 1k\Omega \rightarrow \tau = 0.1\text{초}$$


$$R = 2k\Omega \rightarrow \tau = 0.2\text{초}$$

$$R = 10k\Omega \rightarrow \tau = 1\text{초}$$

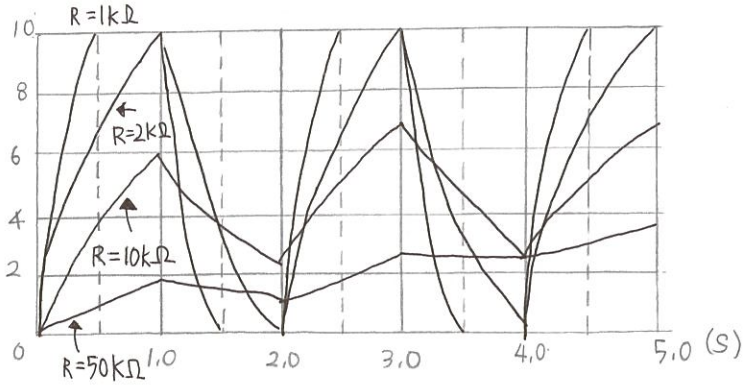
$$R = 50k\Omega \rightarrow \tau = 5\text{초}$$



48 ~ 53

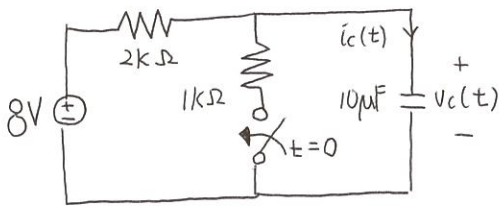


48. $t = 0^-$

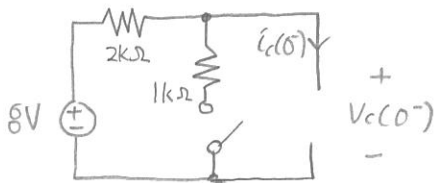

$$i_c(0^-) = 0[A]$$

$$V_c(0^-) = 8[V]$$


49. $t = 0^+$

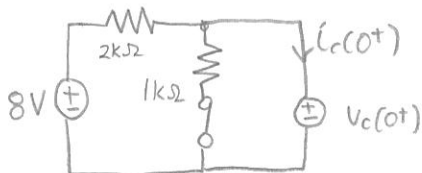

$$V_c(0^+) = V_c(0^-) = 8[V]$$

$$i_c(0^+) = \frac{8 - V_c(0^+)}{2k} - \frac{V_c(0^+)}{1k} = -8[mA]$$


50. $t = \infty$

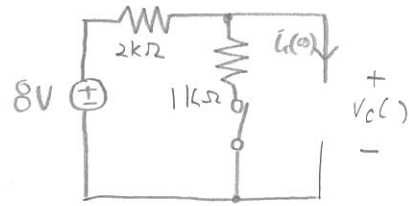

$$V_c(\infty) = 8 \times \frac{1}{2+1} = \frac{8}{3}[V]$$

$$i_c(\infty) = 0[A]$$

51. $t \geq 0 \Rightarrow$ KVL

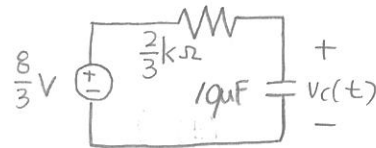

$$\frac{8}{3} = \frac{2}{3} \times 10^3 i_c(t) + V_c(t)$$

$$i_c(t) = 10 \times 10^{-6} \frac{dV_c(t)}{dt}$$

$$\Rightarrow 400 = 150V_c(t) + \frac{dV_c(t)}{dt}$$

커패시터는 연속 $V_c(0^+) = V_c(0^-) = 8[V]$

라플라스 $\Rightarrow sV(s) - 8 + 150V(s) = \frac{400}{s}$

$$V(s) = \frac{8}{s+150} + \frac{400}{s(s+150)}$$

$$= \frac{8}{s+150} + \frac{8}{3} \left(\frac{1}{s} - \frac{1}{s+150} \right)$$

$$= \frac{16}{3} \frac{1}{s+150} + \frac{8}{3} \frac{1}{s}$$

$$V_c(t) = \frac{8}{3} + \frac{16}{3} e^{-150t} [V], t > 0$$

$$i_c(t) = 10 \times 10^{-6} \times \frac{dV_c(t)}{dt}$$

$$= 10 \times 10^{-6} \times \frac{16}{3} \times (-150) e^{-150t}$$


$$= -8e^{-150t} [mA] \quad t > 0$$

$$52 \quad r = \frac{1}{150} \text{ 초}$$



$$5r = \frac{1}{30} \text{ 초} \quad \text{후 정상 도달}$$

$$53 \quad v_c(t) = \frac{8}{3} + \frac{16}{3} e^{-150t} \text{ [V]}, t \geq 0$$
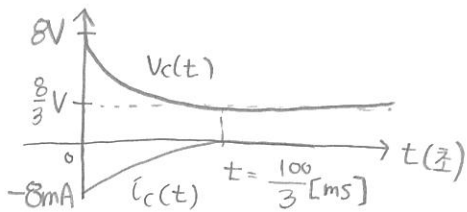
$$i_c(t) = \begin{cases} 0, & t = 0^- \\ -8e^{-150t}, & t > 0 \end{cases} \text{ [mA]}$$




54 ~ 57

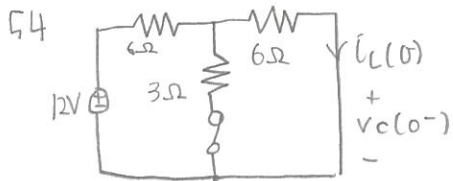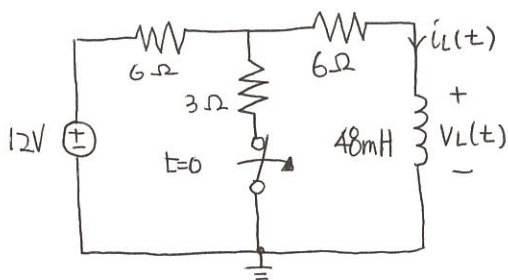

$$i_L(0^-) = \frac{12}{6+2} \times \frac{3}{3+6} = \frac{1}{2} \text{ [A]}$$

$$v_L(0^-) = 0 \text{ [V]}$$

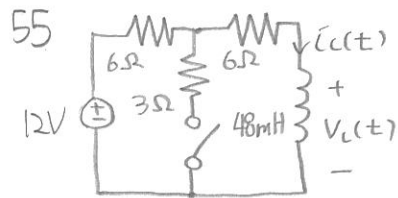

$$\text{KVL} \Rightarrow 12 = 12 i_c(t) + 48 \times 10^{-3} \frac{di_L(t)}{dt}$$

$$\frac{di_L(t)}{dt} + 250 i_L(t) = 250$$

$$i_L(0^+) = i_L(0^-) = \frac{1}{2} \text{ [A]}$$

$$\text{라플라스} \Rightarrow s I_L(s) - \frac{1}{2} + 250 I_L(s) = \frac{250}{s}$$

$$I_L(s) = \frac{250}{s(s+250)} + \frac{1}{2} \left(\frac{1}{s+250} \right)$$

$$= \frac{1}{s} - \frac{1}{2} \left(\frac{1}{s+250} \right)$$

$$I_L(t) = 1 - \frac{1}{2} e^{-250t} \text{ [A]}, t > 0$$

$$v_c(t) = 48 \times 10^{-3} \frac{di_L(t)}{dt}$$

$$= 48 \times 10^{-3} \times \frac{1}{2} \times 250 e^{-250t}$$


$$= 6 e^{-250t} \text{ [V]}, t > 0$$

$$56. \text{ 시정수 } r = \frac{48 \times 10^{-3}}{12} = 0.004 \text{ [s]}$$


$$5r = 0.02 \text{ [s]} \quad \text{후 정상 도달}$$

$$57. i_L(t) = 1 - \frac{1}{2} e^{-250t} \text{ [A]}, t \geq 0$$
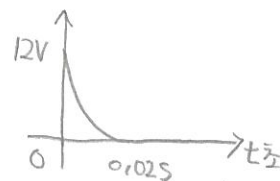
$$v_L(t) = \begin{cases} 0, & t = 0^- \\ 6e^{-250t}, & t > 0 \end{cases} \text{ [V]}, t > 0$$



$v_L(t)$ 그래프

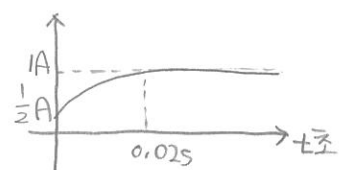

$i_L(t)$ 그래프